
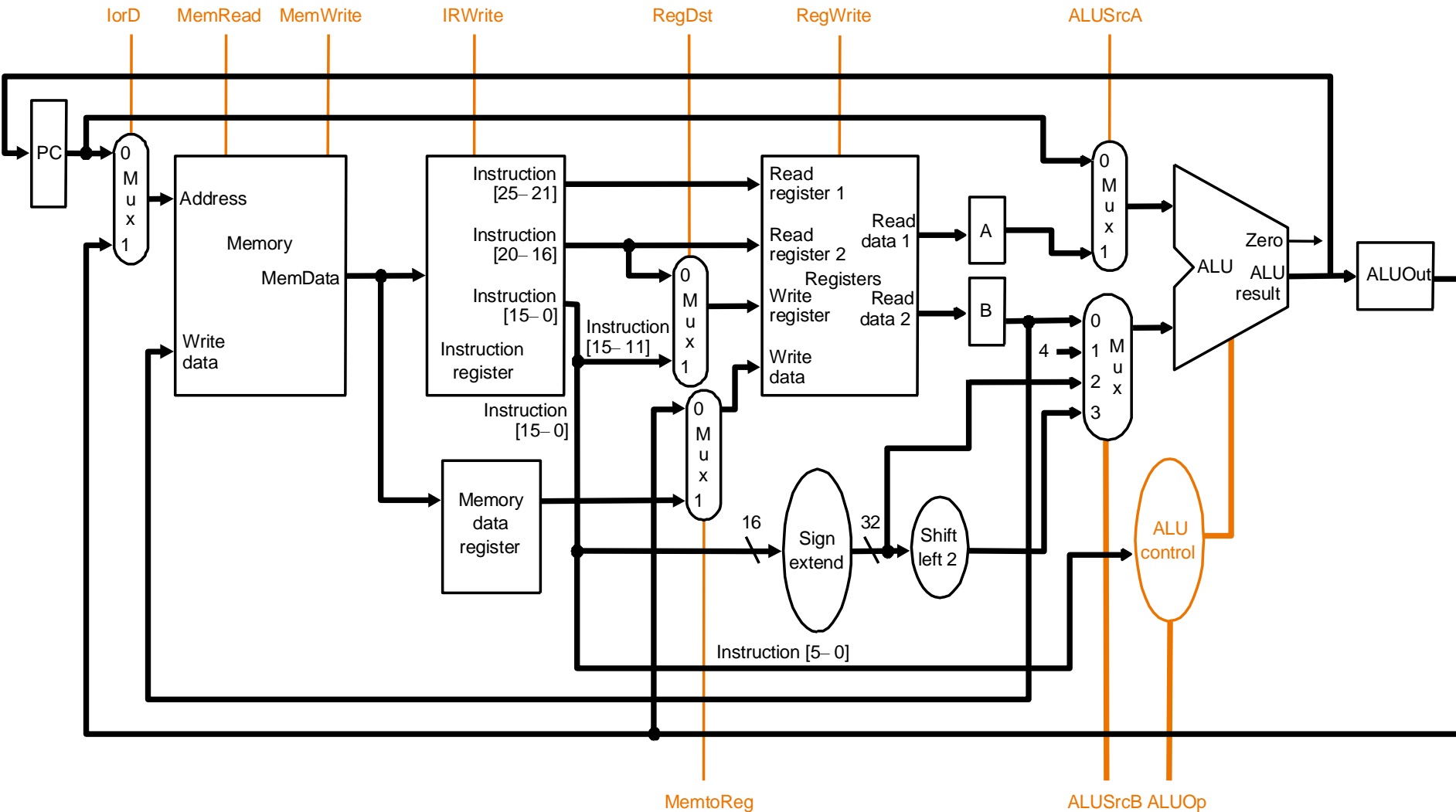


# Multicycle Datapath with Control I

 

... with control lines and the ALU control block added – *not all* control lines are shown


# Multicycle Datapath with Control II



Complete multicycle MIPS datapath (with branch and jump capability) and showing the main control block and all control lines


# Multicycle Control Step (1): Fetch

IR = Memory[PC];  
PC = PC + 4;

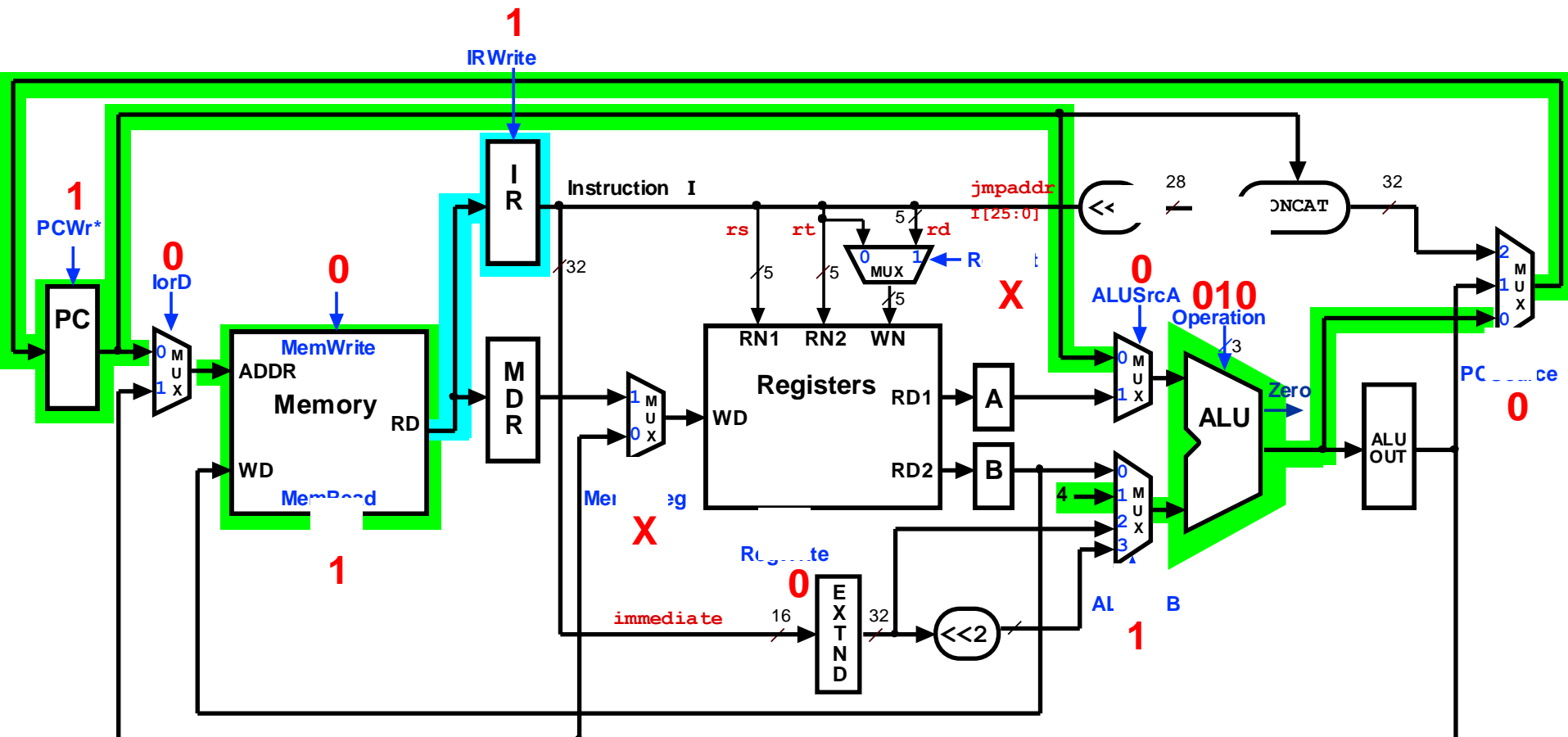

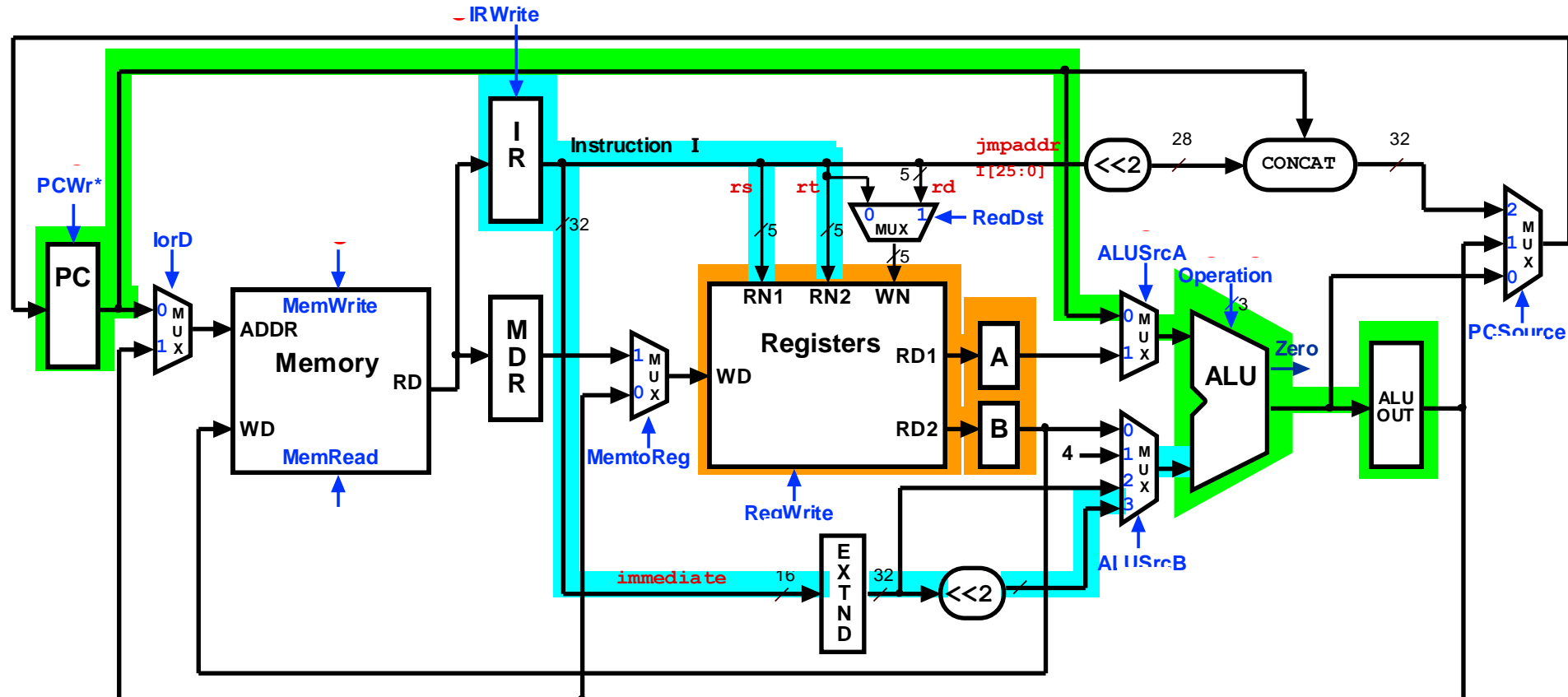
# Multicycle Control Step (2): Instruction Decode & Register Fetch

$A = \text{Reg}[\text{IR}[25-21]];$                        $(A = \text{Reg}[\text{rs}])$   
 $B = \text{Reg}[\text{IR}[20-15]];$                        $(B = \text{Reg}[\text{rt}])$   
 $\text{ALUOut} = (\text{PC} + \text{sign-extend}(\text{IR}[15-0]) \ll 2);$




# Multicycle Datapath with Control II

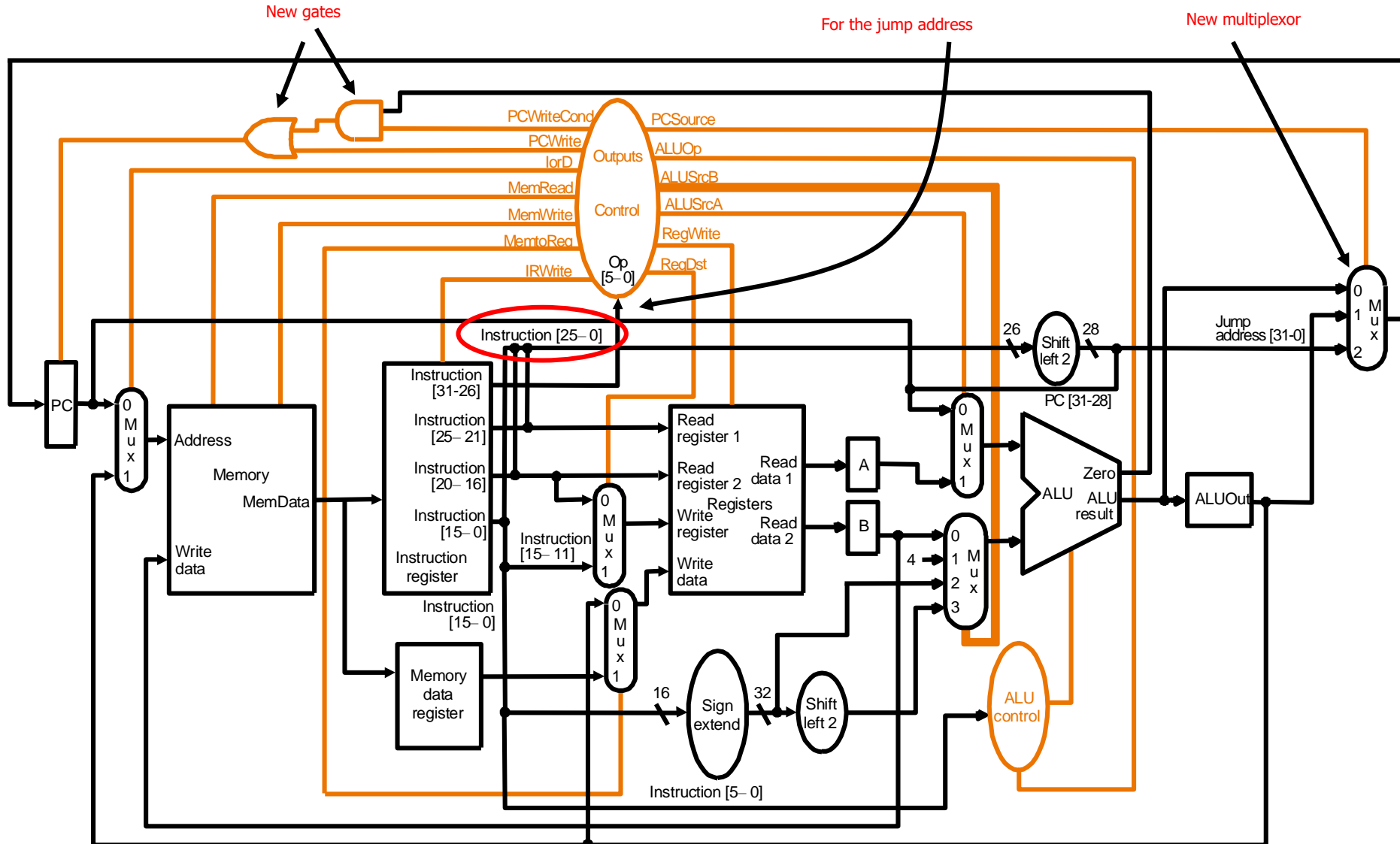

Complete multicycle MIPS datapath (with branch and jump capability) and showing the main control block and all control lines

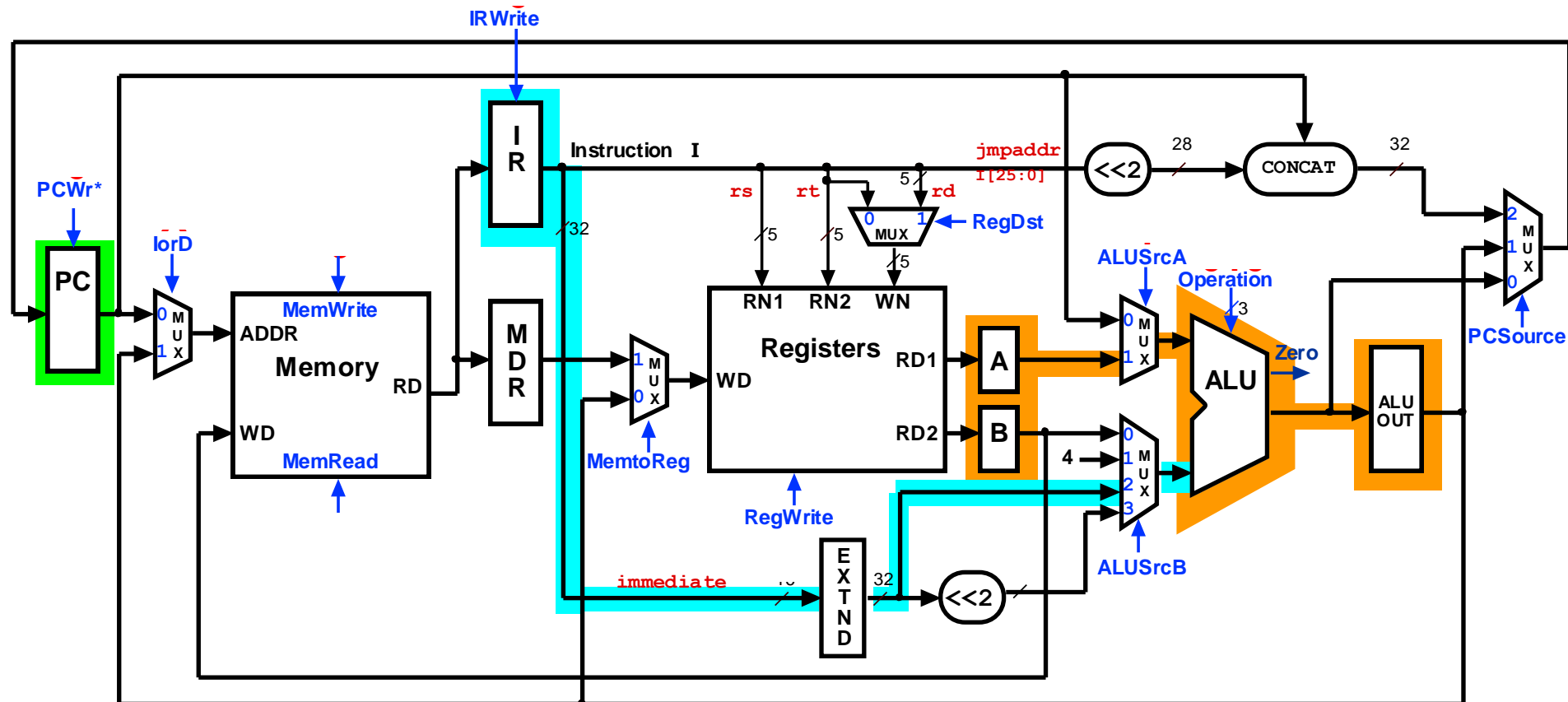
# Multicycle Control Step (3): Memory Reference Instructions

$$\text{ALUOut} = A + \text{sign-extend}(\text{IR}[15:0]);$$




# Multicycle Control Step (3): ALU Instruction (R-Type)

ALUOut = A op B;

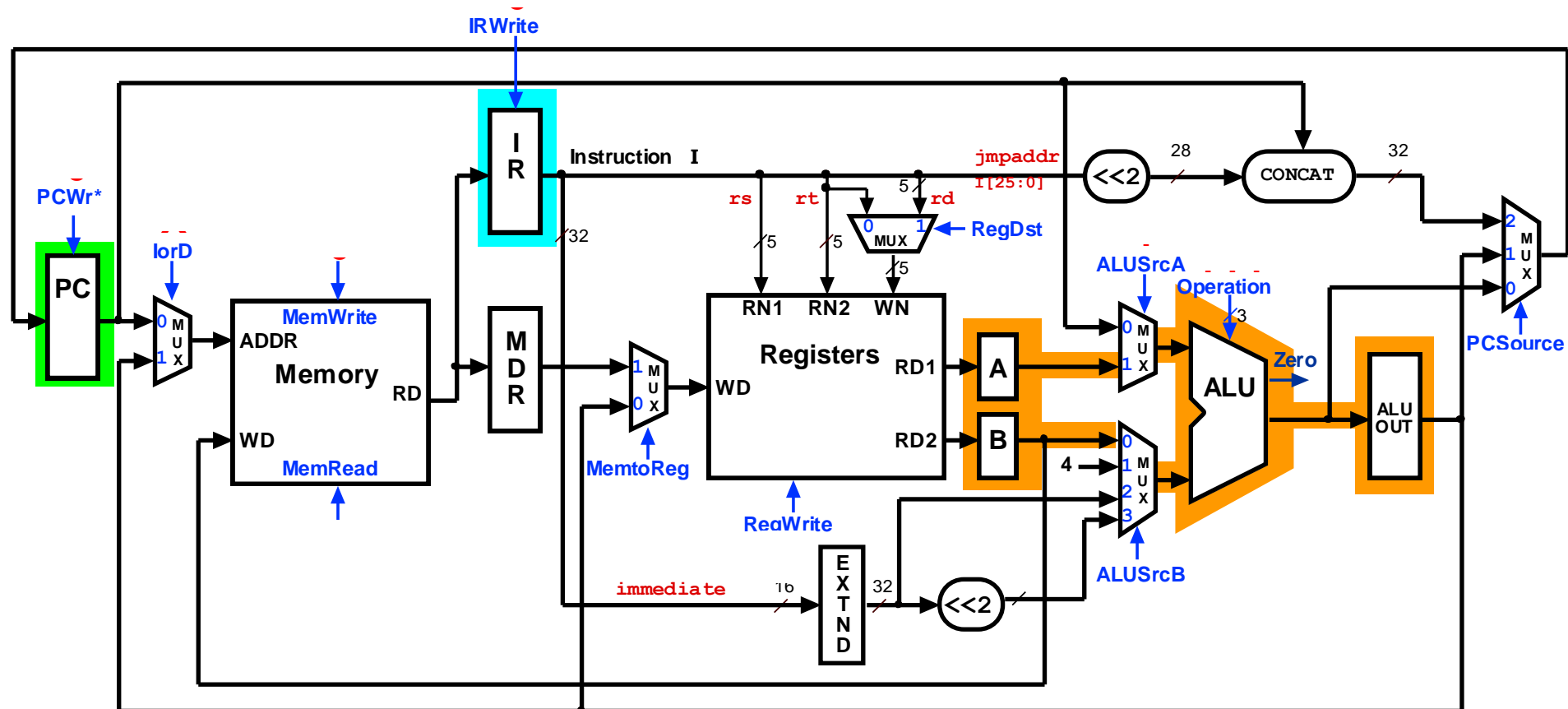

# Multicycle Control Step (3): Branch Instructions


if (A == B) PC = ALUOut;

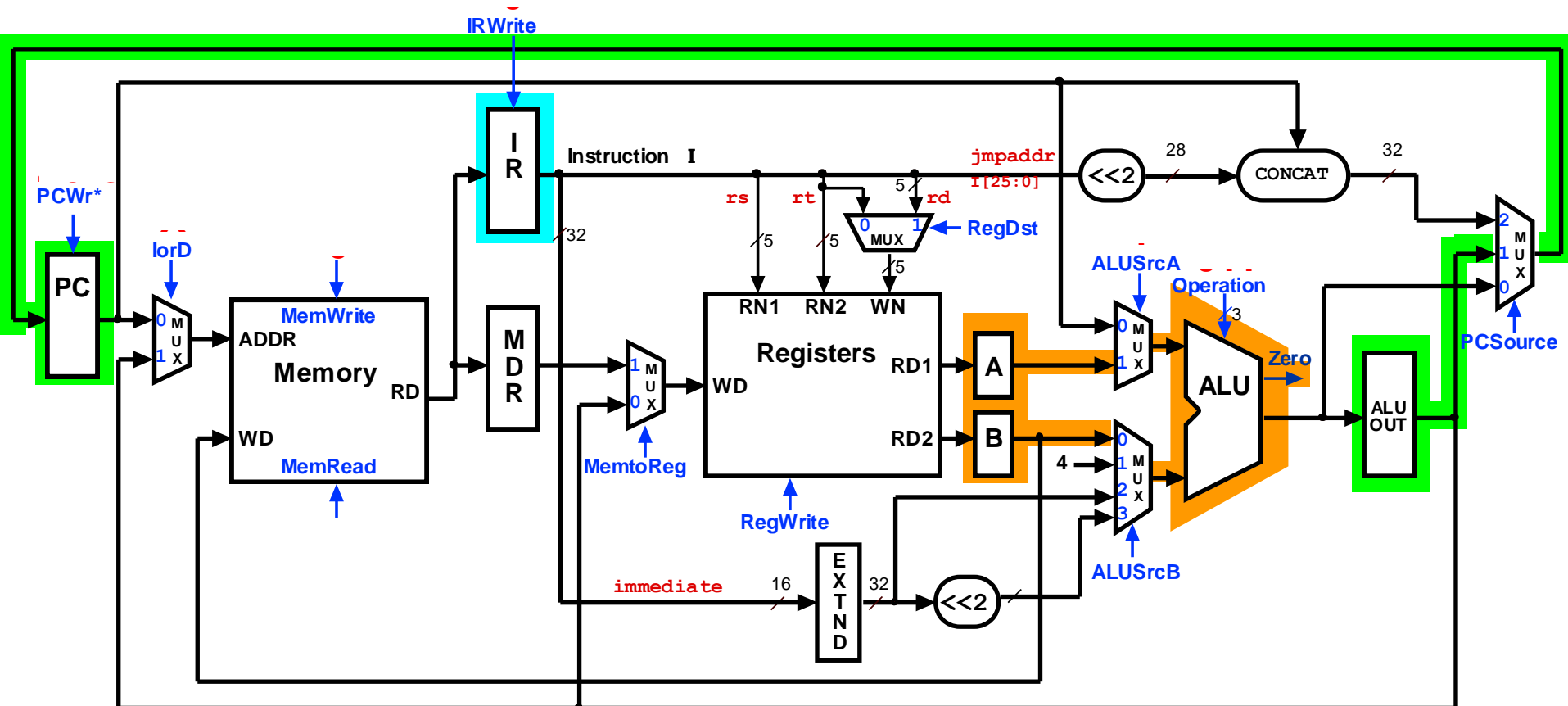



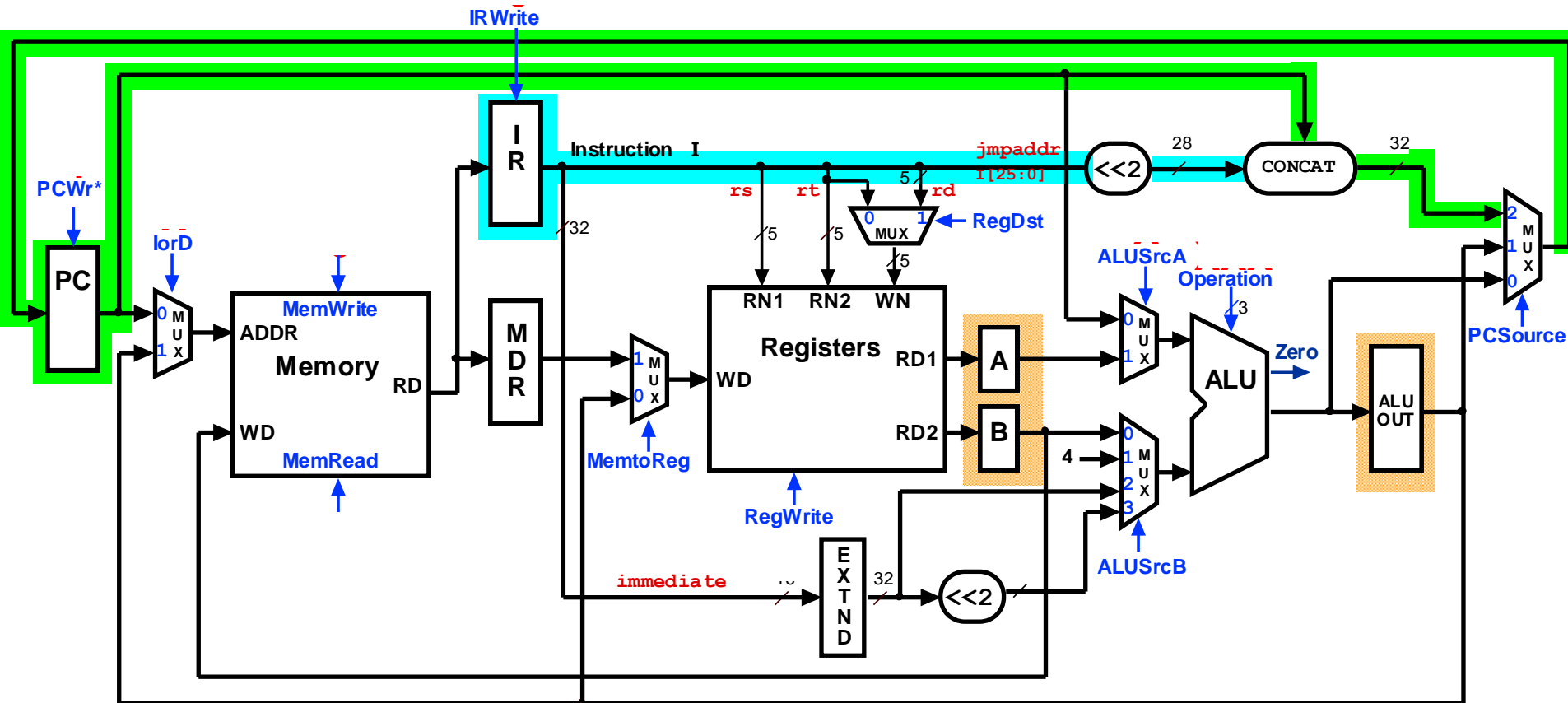
# Multicycle Execution Step (3): Jump Instruction

$PC = PC[21-28] \text{ concat } (IR[25-0] \ll 2);$



# Multicycle Control Step (4): Memory Access - Read ( $1_W$ )


MDR = Memory[ALUOut];

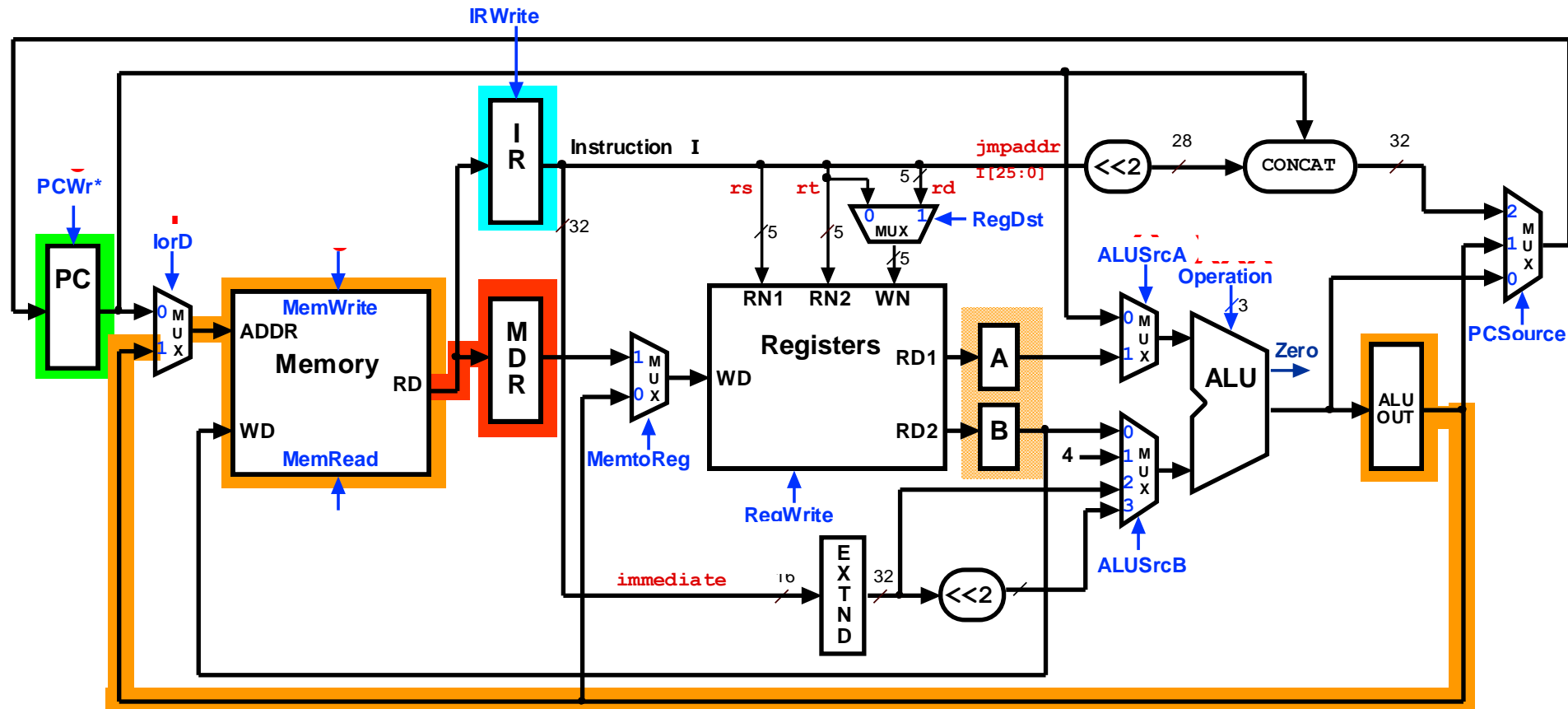

# Multicycle Execution Steps (4)


## Memory Access - Write (sw)

Memory[ALUOut] = B;

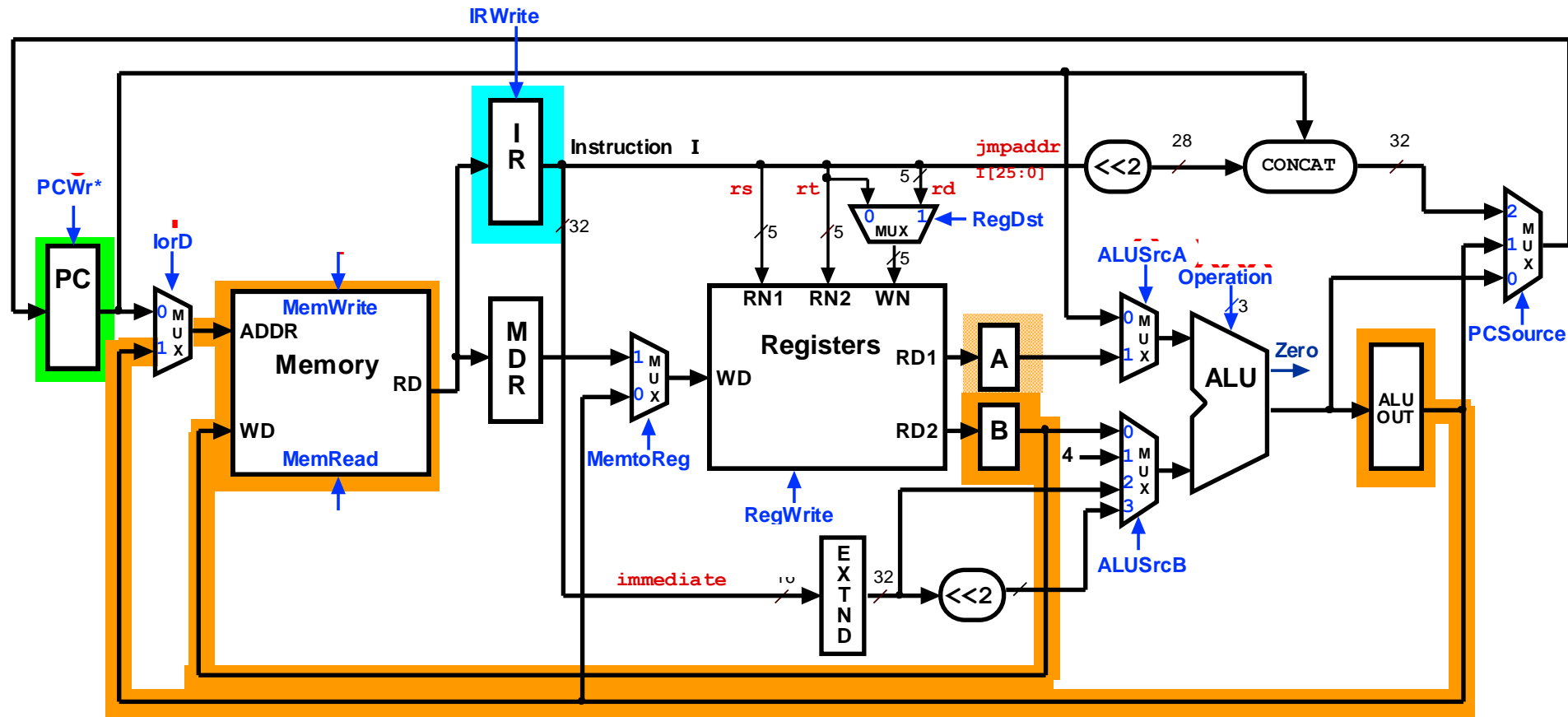

# Multicycle Control Step (4): ALU Instruction (R-Type)


(Reg[Rd] = ALUOut)

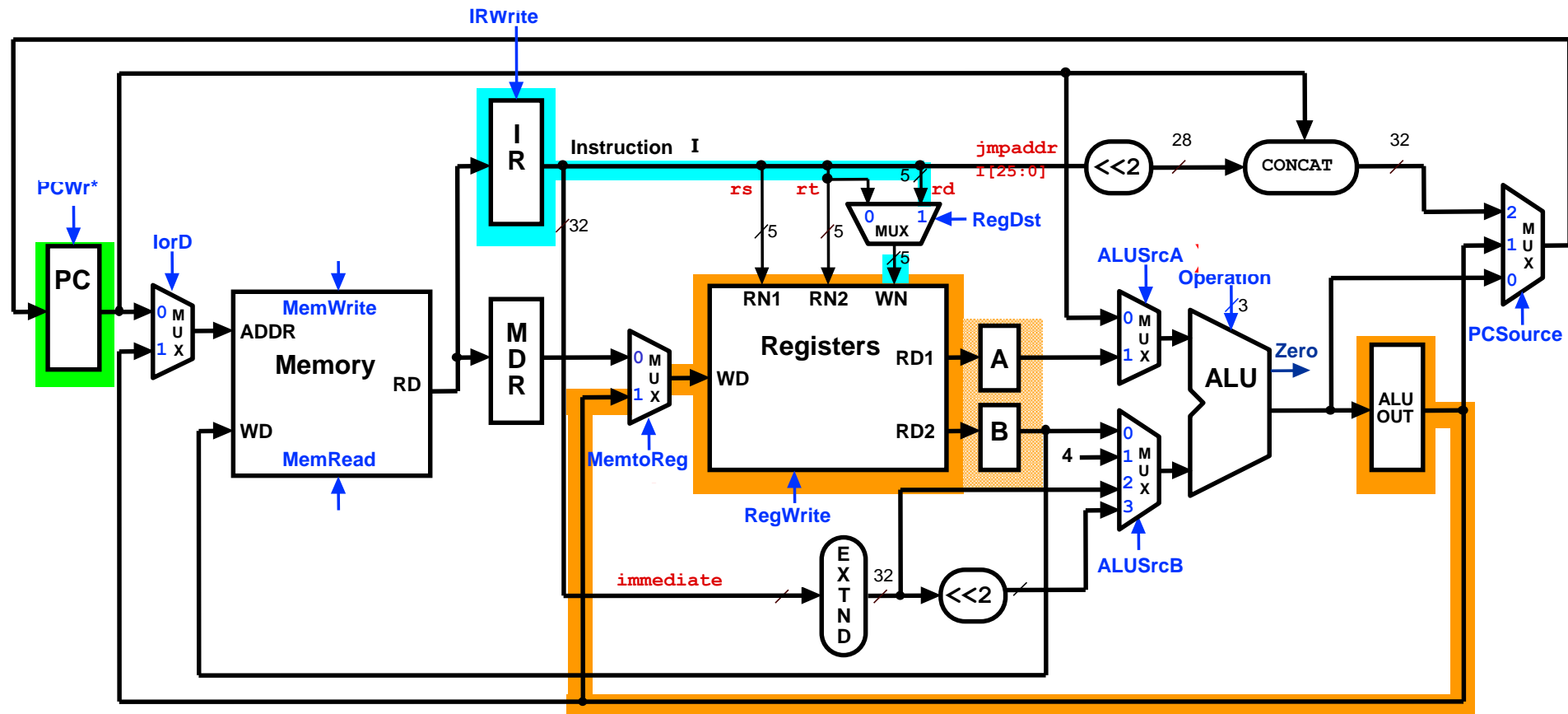

# Multicycle Execution Steps (5)
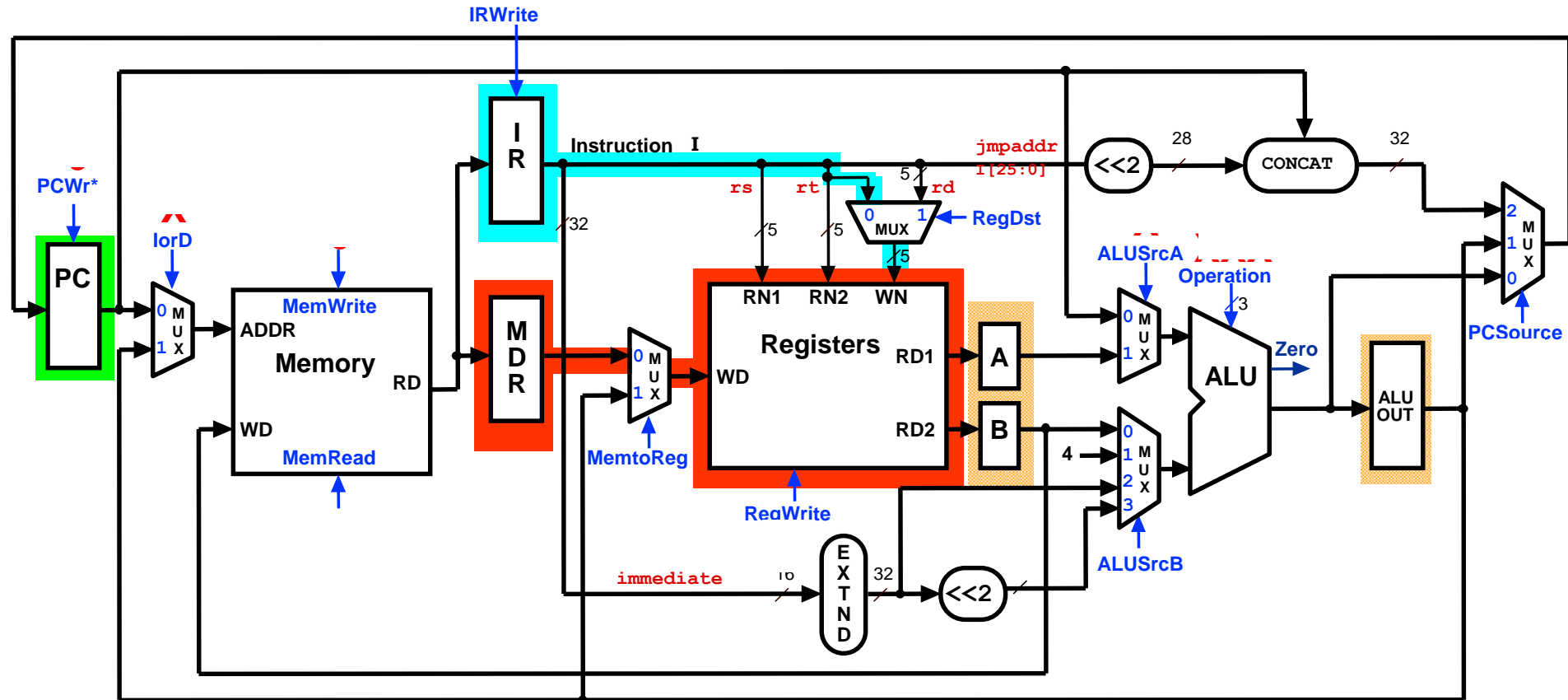
## Memory Read Completion (lw)

$\text{Reg}[\text{IR}[20-16]] = \text{MDR};$




# Implementing Control

- Value of control signals is dependent upon:
  - what instruction is being executed
  - which step is being performed
- Use the information we have accumulated to specify a finite state machine
  - specify the finite state machine graphically, or
  - use microprogramming
- Implementation is then derived from the specification

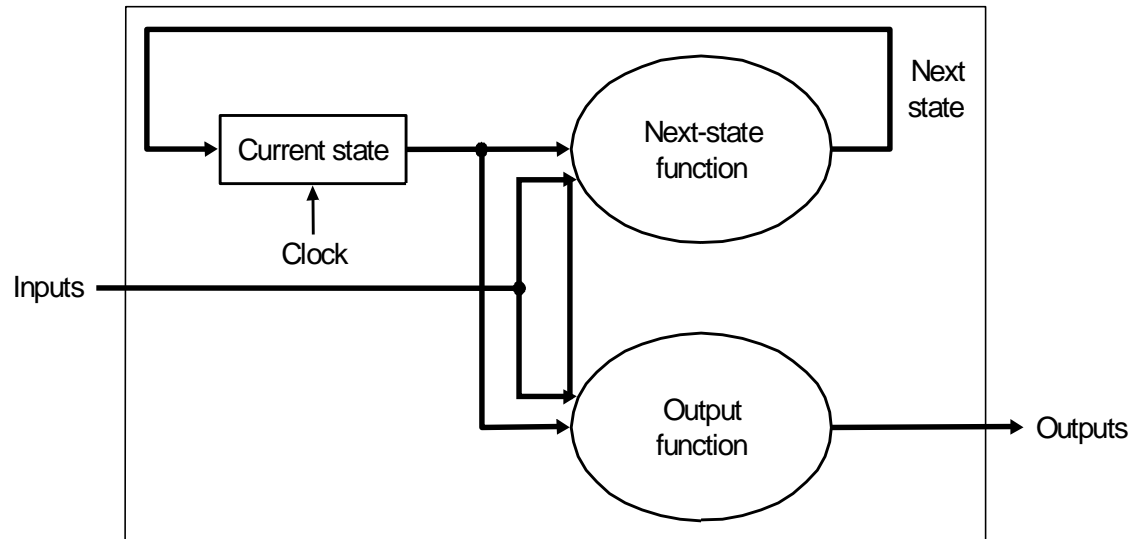
# Review: Finite State Machines

- Finite state machines (FSMs):
  - a set of states and
  - next state function, determined by current state and the input
  - output function, determined by current state and possibly input




- We'll use a *Moore machine* – output based *only* on current state

# FSM Control: High-level View

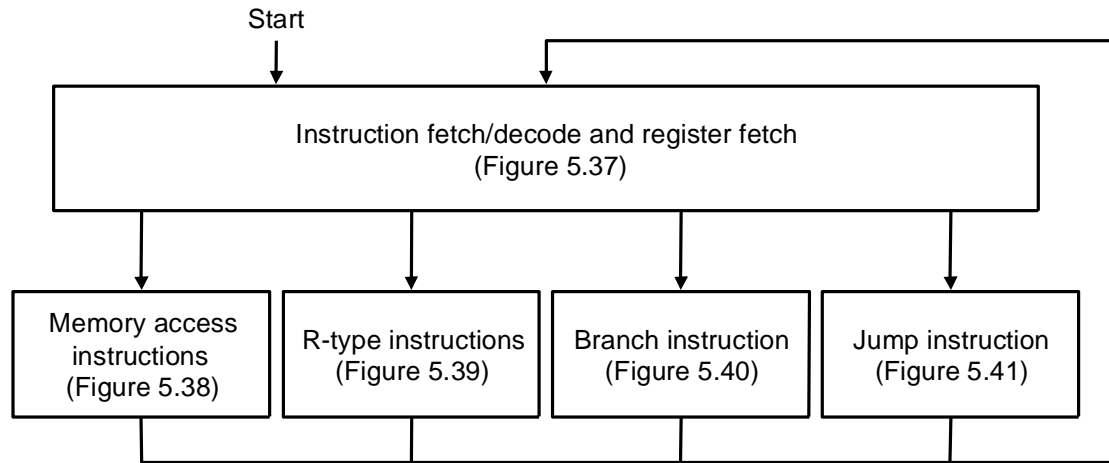
 
## High-level view of FSM control


**Asserted signals  
shown inside  
state circles**




**Instruction fetch and decode steps of every instruction is identical**



# FSM Control: Complete View

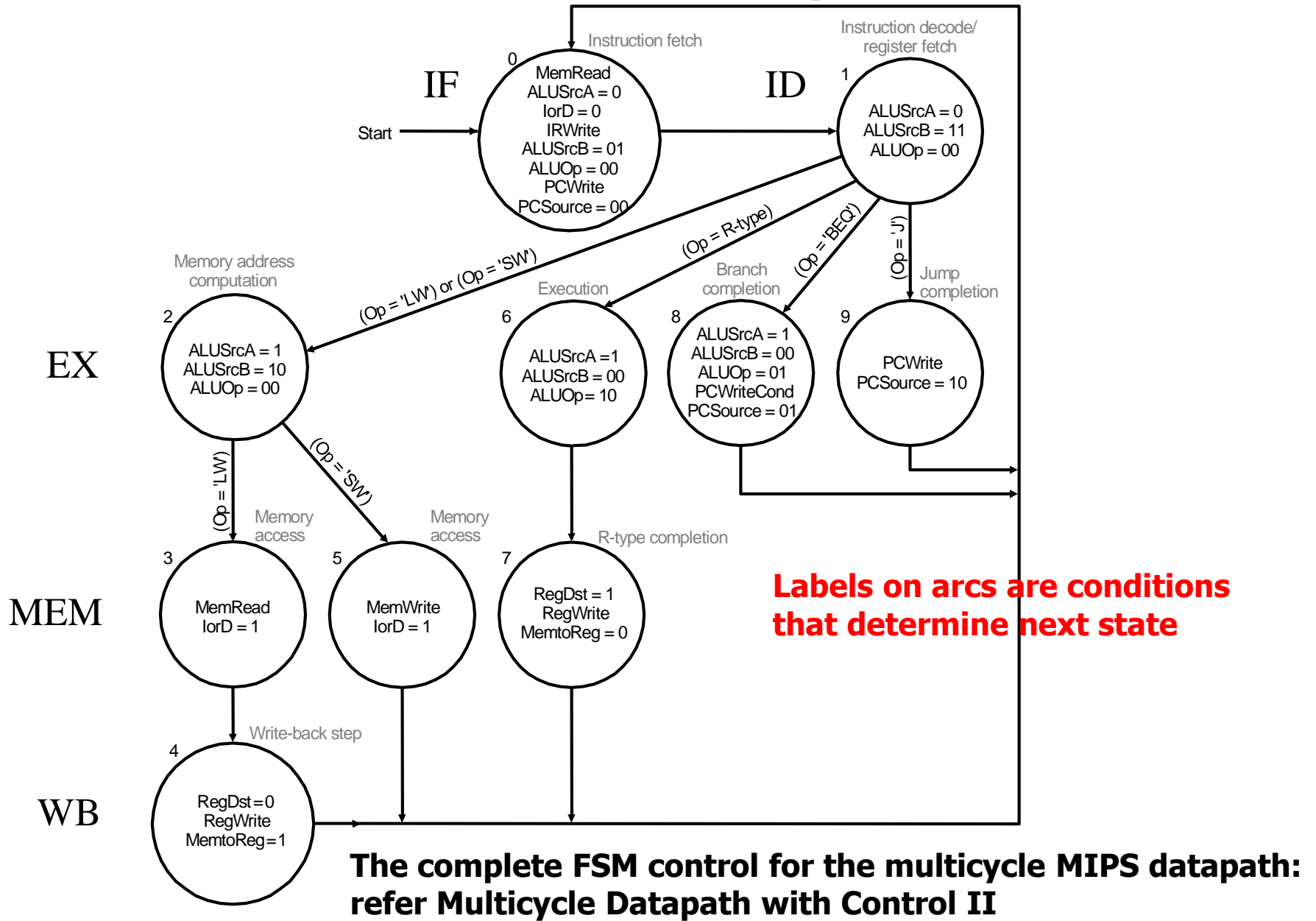


# FSM Control: Implementation

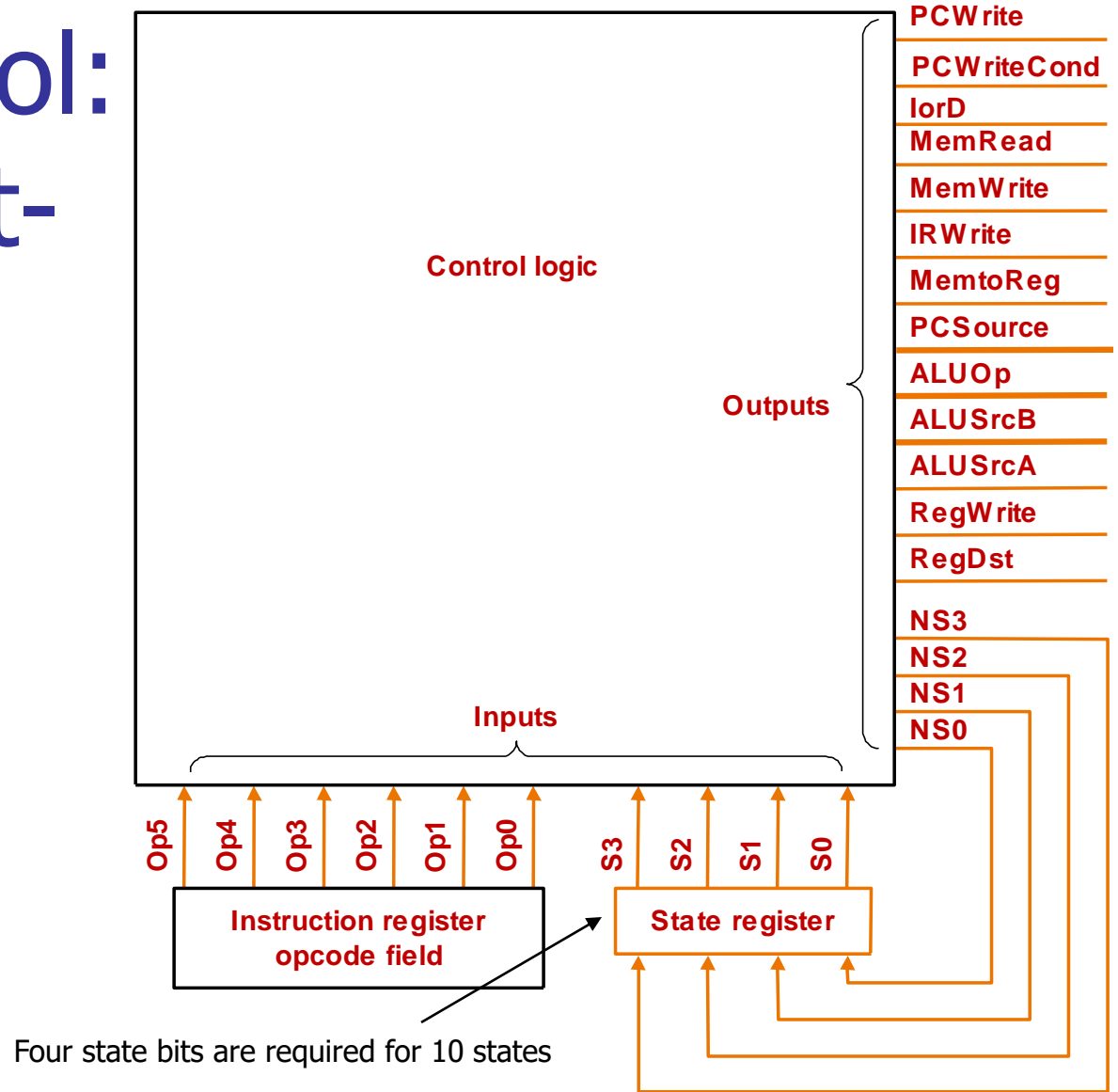

**High-level view of FSM implementation: inputs to the combinational logic block are the current state number and instruction opcode bits; outputs are the next state number and control signals to be asserted for the current state**

# FSM Control: PLA Implementation

 

Upper half is the AND plane that computes all the products. The products are carried to the lower OR plane by the vertical lines. The sum terms for each output is given by the corresponding horizontal line

E.g.,  $IorD = S0.S1.S2.S3 + S0.S1.S2.\bar{S3}$