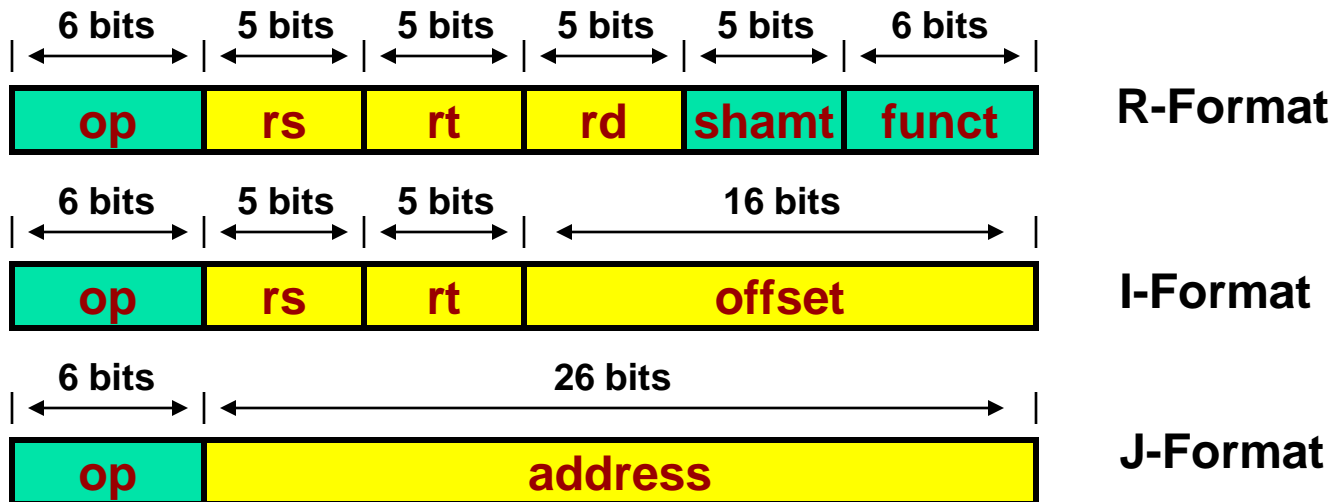


The Processor: Datapath and Control


Implementing MIPS

- We're ready to look at an implementation of the MIPS instruction set
- Simplified to contain *only*
 - arithmetic-logic instructions: `add`, `sub`, `and`, `or`, `slt`
 - memory-reference instructions: `lw`, `sw`
 - control-flow instructions: `beq`, `j`



Implementing MIPS: the Fetch/Execute Cycle

 - High-level abstract view of *fetch/execute* implementation
 - use the program counter (PC) to read instruction address
 - *fetch* the instruction from memory and increment PC
 - use fields of the instruction to select registers to read
 - *execute* depending on the instruction
 - repeat...



Overview: Processor Implementation Styles


- Single Cycle
 - perform each instruction in 1 clock cycle
 - clock cycle must be long enough for slowest instruction; therefore,
 - disadvantage: only as fast as slowest instruction
- Multi-Cycle
 - break fetch/execute cycle into multiple steps
 - perform 1 step in each clock cycle
 - advantage: each instruction uses only as many cycles as it needs
- Pipelined
 - execute each instruction in multiple steps
 - perform 1 step / instruction in each clock cycle
 - process multiple instructions in parallel – assembly line

Functional Elements



- Two types of functional elements in the hardware:
 - elements that *operate on* data (called *combinational elements*)
 - elements that *contain* data (called *state* or *sequential elements*)

Combinational Elements

 - Works as an *input \Rightarrow output function*, e.g., ALU
- Combinational logic *reads input data from one register and writes output data to another, or same, register*
 - *read/write happens in a single cycle* – combinational element *cannot store data* from one cycle to a future one



Combinational logic hardware units

  


State Elements

- State elements contain *data* in internal storage, e.g., *registers* and *memory*
- All state elements together *define* the *state of the machine*
- *Flipflops* and *latches* are 1-bit state elements, equivalently, they are *1-bit memories*
- The *output(s)* of a flipflop or latch *always* depends on the bit value stored, i.e., its state, and can be called *1/0* or *high/low* or *true/false*
- The *input* to a flipflop or latch can change its state depending on whether it is clocked or not...

State Elements on the Datapath: Register File

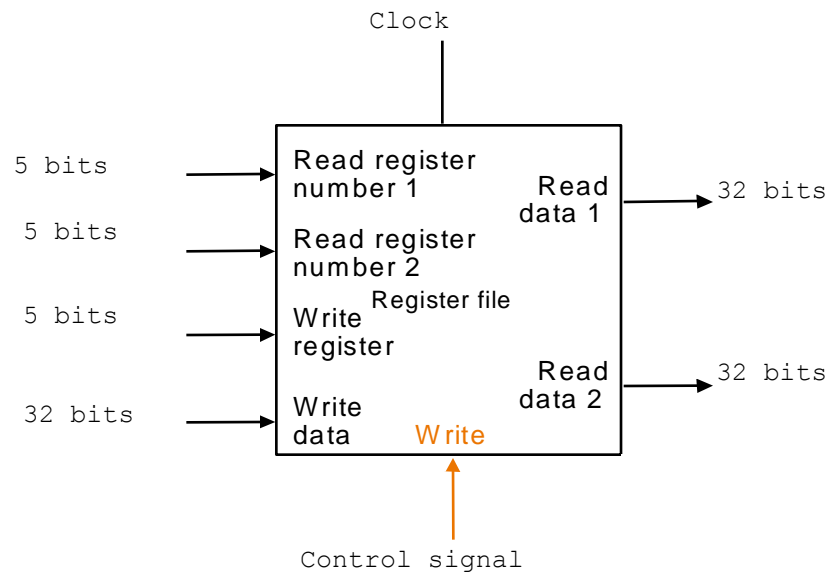
- Registers are implemented with arrays of D-flipflops




Register file with two read ports and one write port

State Elements on the Datapath: Register File

- Port implementation:

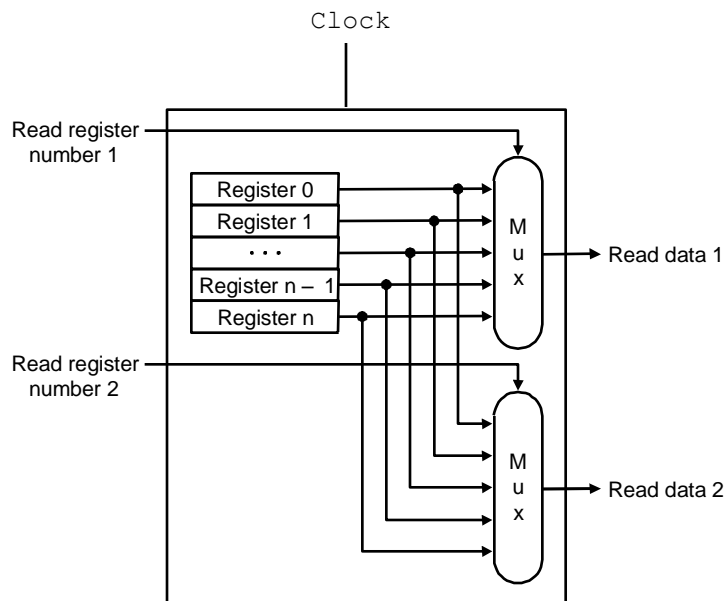

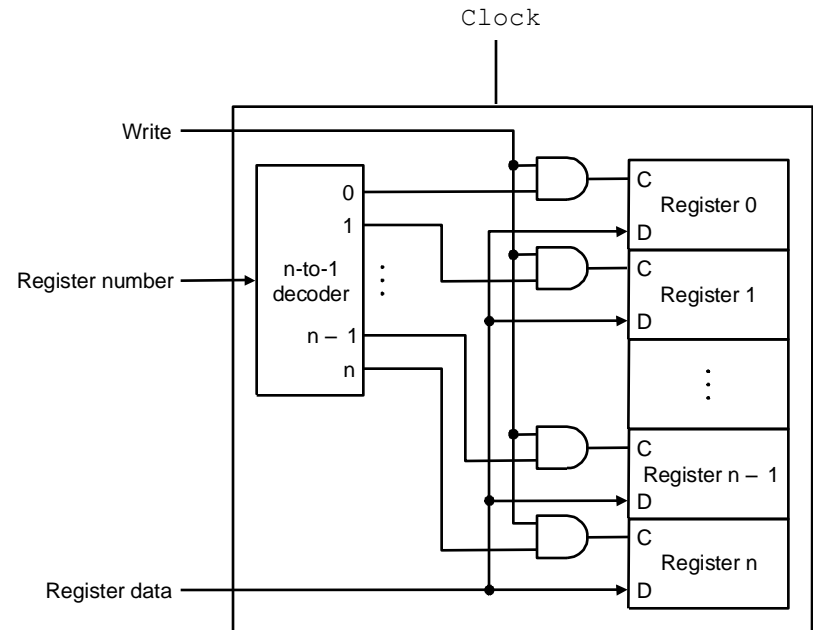Read ports are implemented with a pair of multiplexors – 5 bit multiplexors for 32 registers



Write port is implemented using a decoder – 5-to-32 decoder for 32 registers. Clock is relevant to write as register state may change only at clock edge


Verilog

- All components that we have discussed – and shall discuss – can be fabricated using Verilog

Single-cycle Implementation of MIPS


- Our first implementation of MIPS will use a *single* long clock cycle for every instruction
- Every instruction begins on one up (or, down) clock edge and ends on the next up (or, down) clock edge
- This approach is *not practical* as it is much slower than a *multicycle* implementation where different instruction classes can take different numbers of cycles
 - in a single-cycle implementation every instruction must take the same amount of time as the slowest instruction
 - in a multicycle implementation this problem is avoided by allowing quicker instructions to use fewer cycles
- Even though the single-cycle approach is not practical it is simple and useful to understand first
- *Note* : we shall implement `jump` at the very end

 Datapath: Instruction Store/Fetch & PC Increment




Three elements used to store and fetch instructions and increment the PC


Animating the Datapath

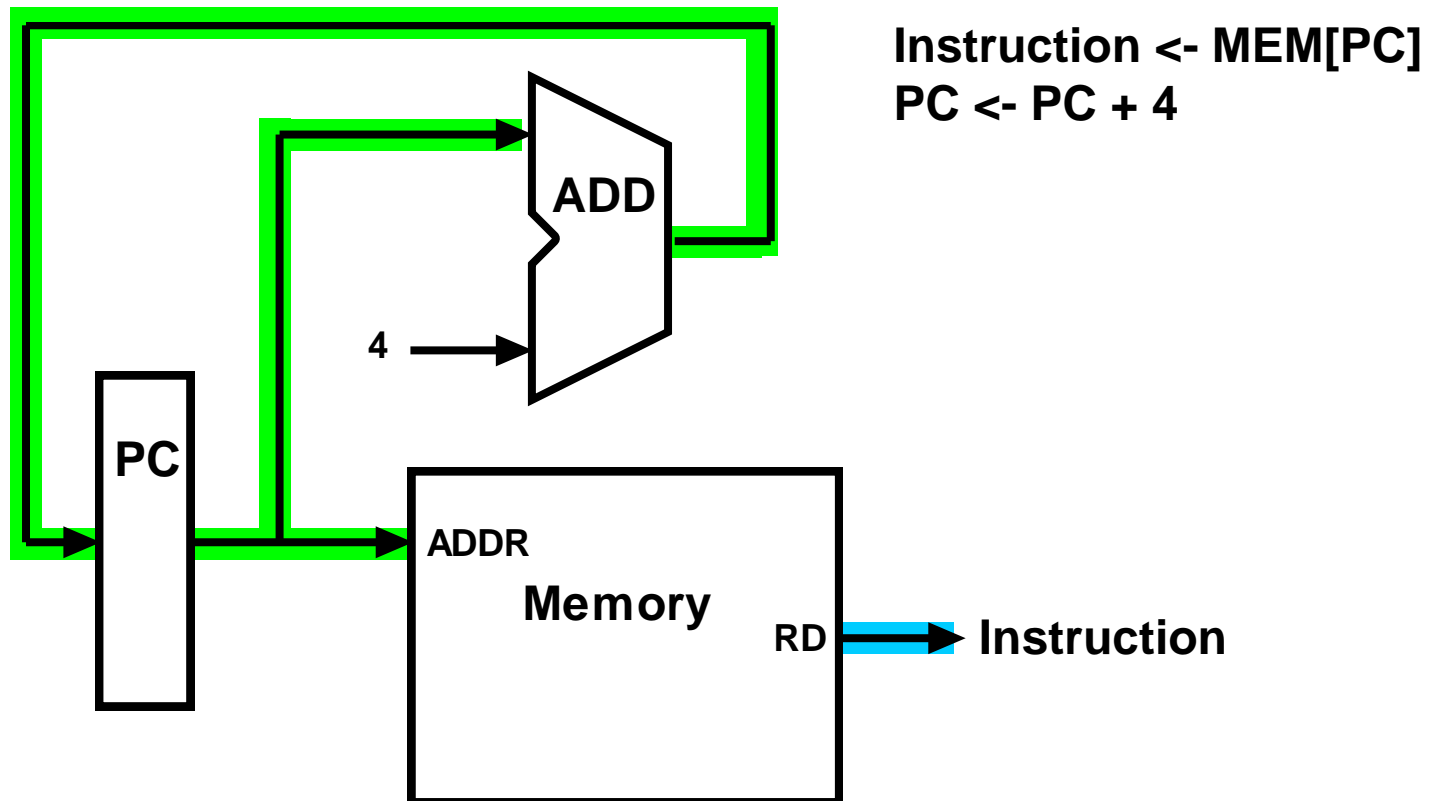


Datapath: R-Type Instruction

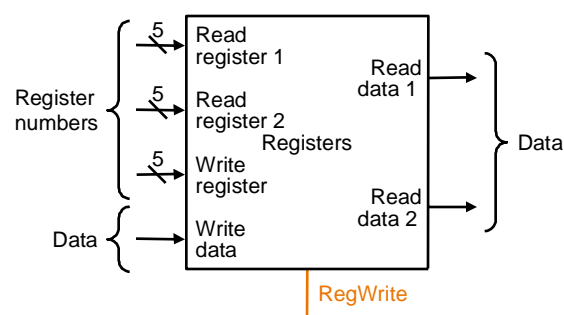

a. Registers

 

b. ALU

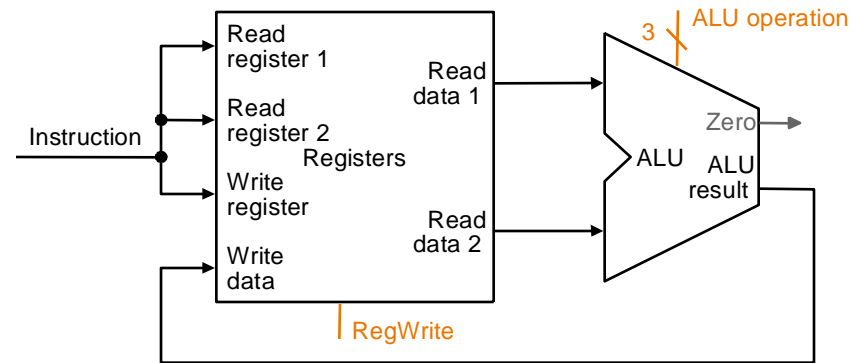

Datapath

Two elements used to implement R-type instructions


Animating the Datapath

Instruction




add rd, rs, rt

$R[rd] \leftarrow R[rs] + R[rt];$

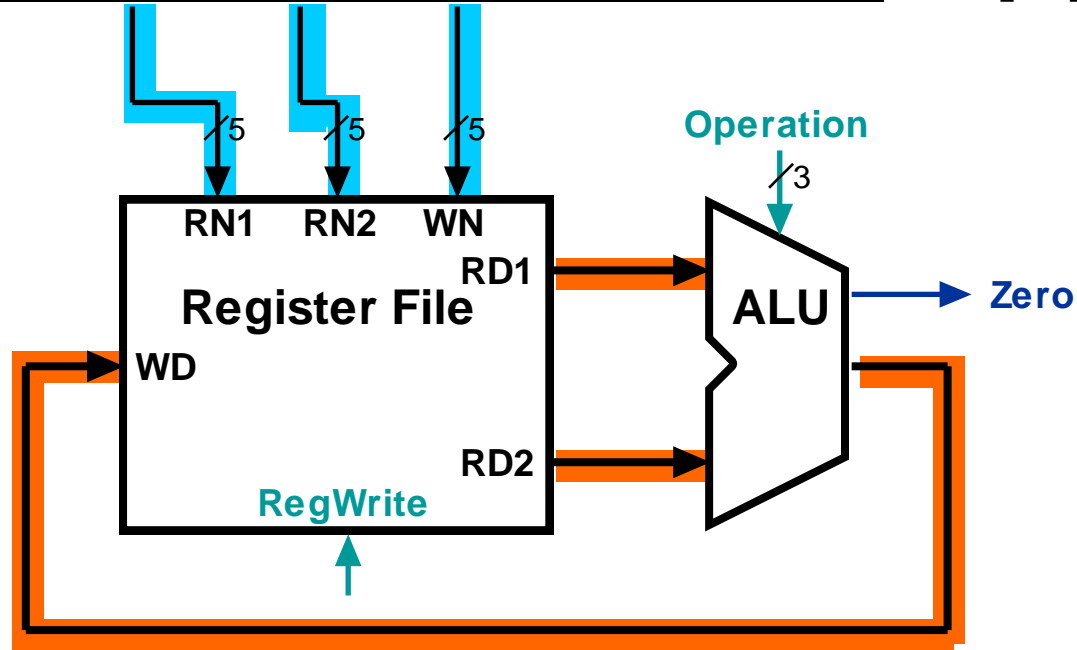


Datapath: Load/Store Instruction

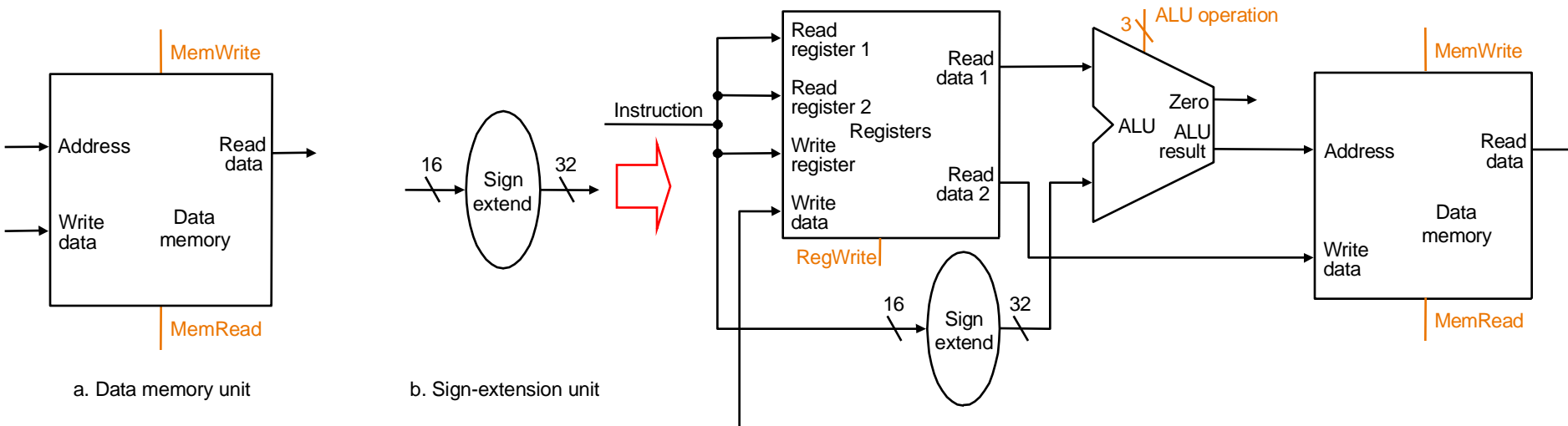


**Two additional elements used
To implement load/stores**

Datapath


Animating the Datapath

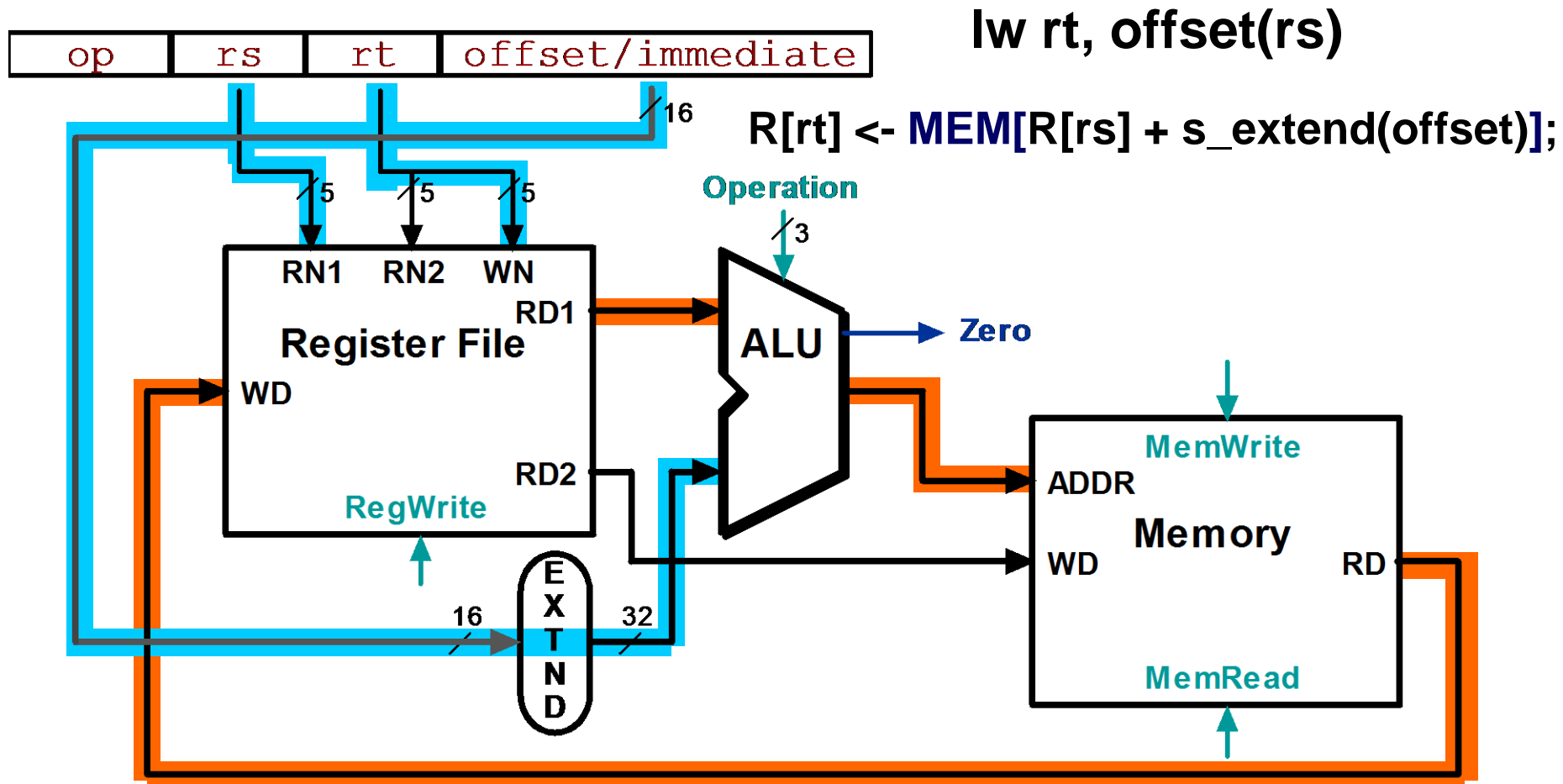


Animating the Datapath

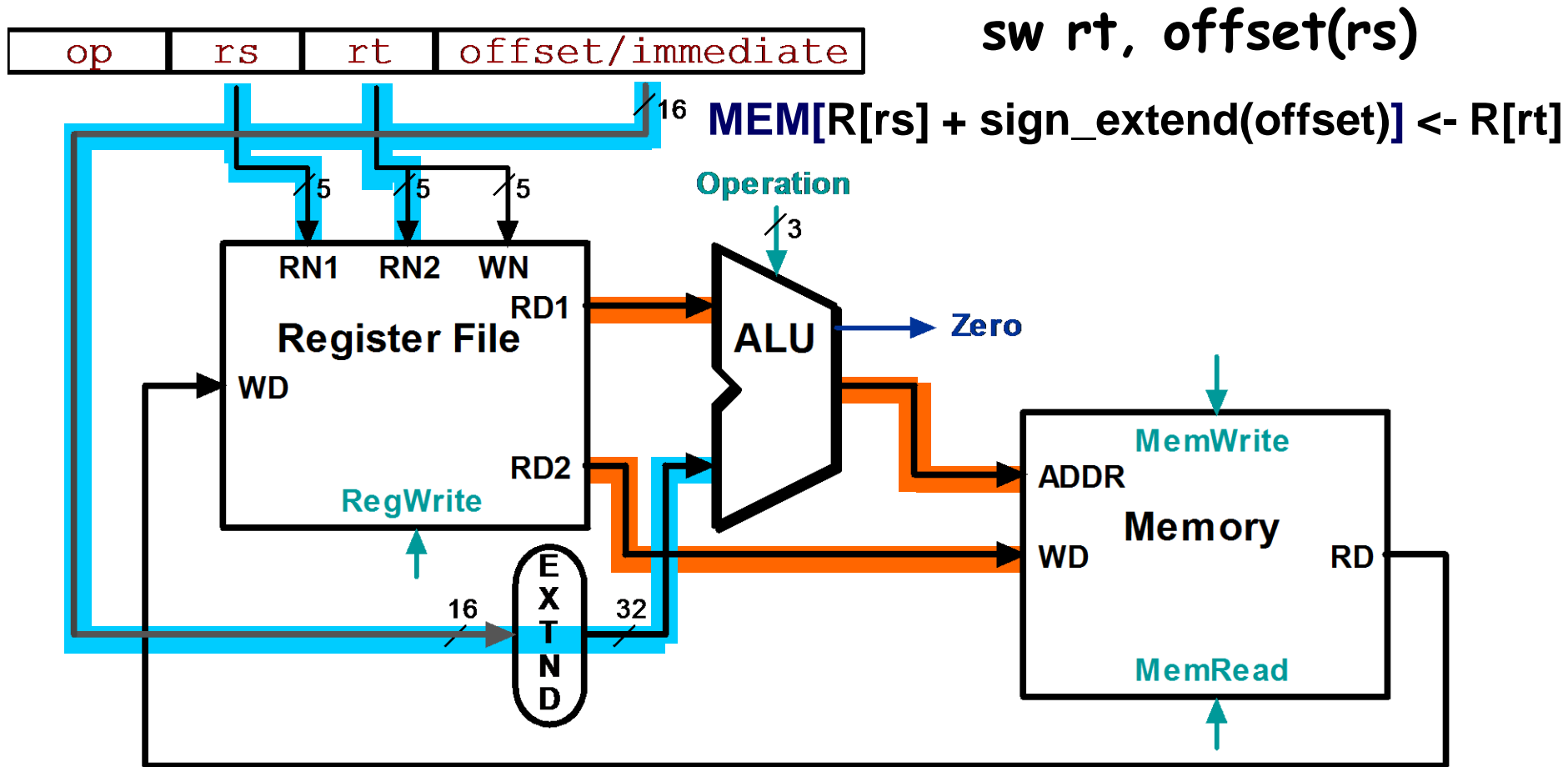


Datapath: Branch Instruction

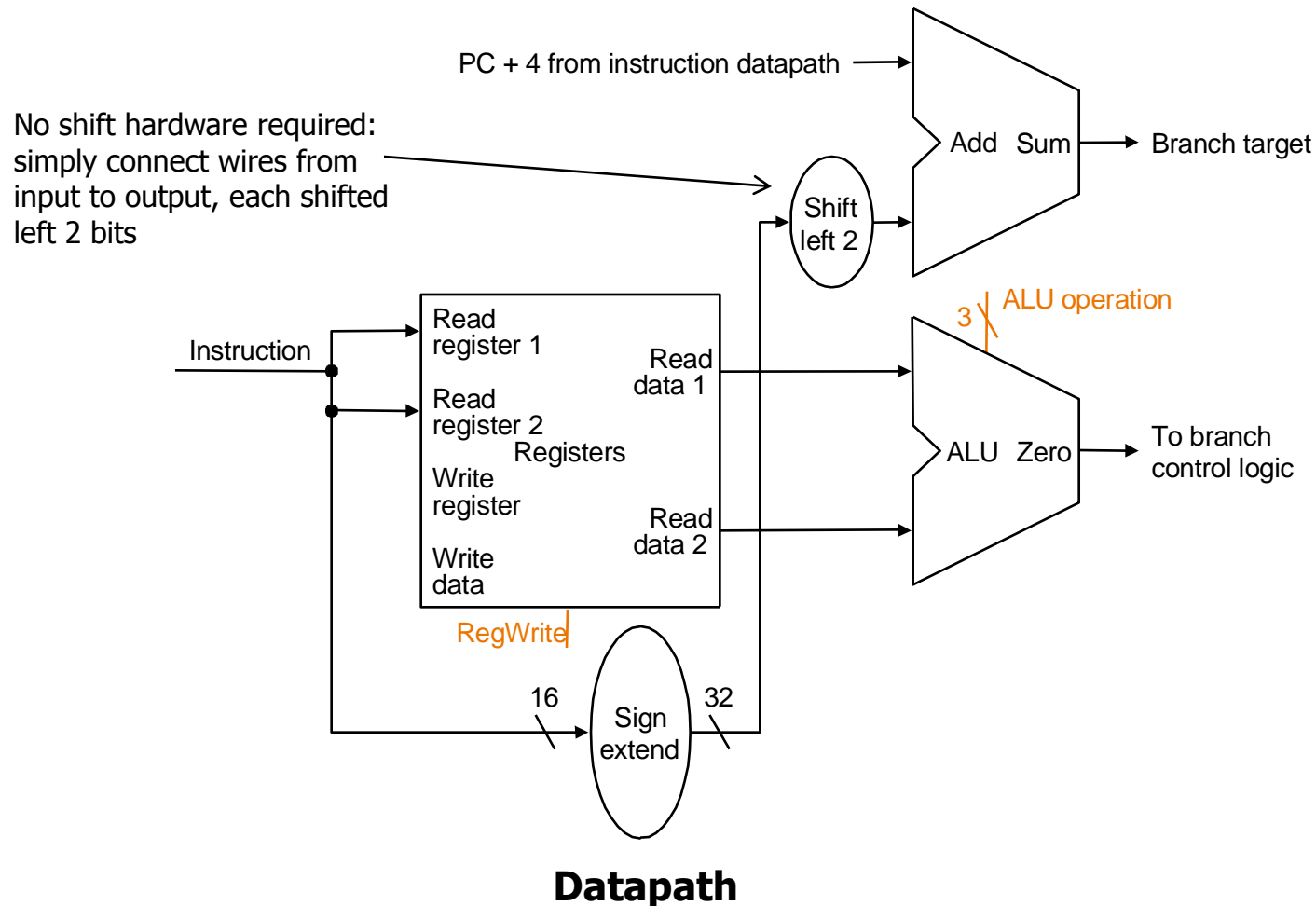

Animating the Datapath

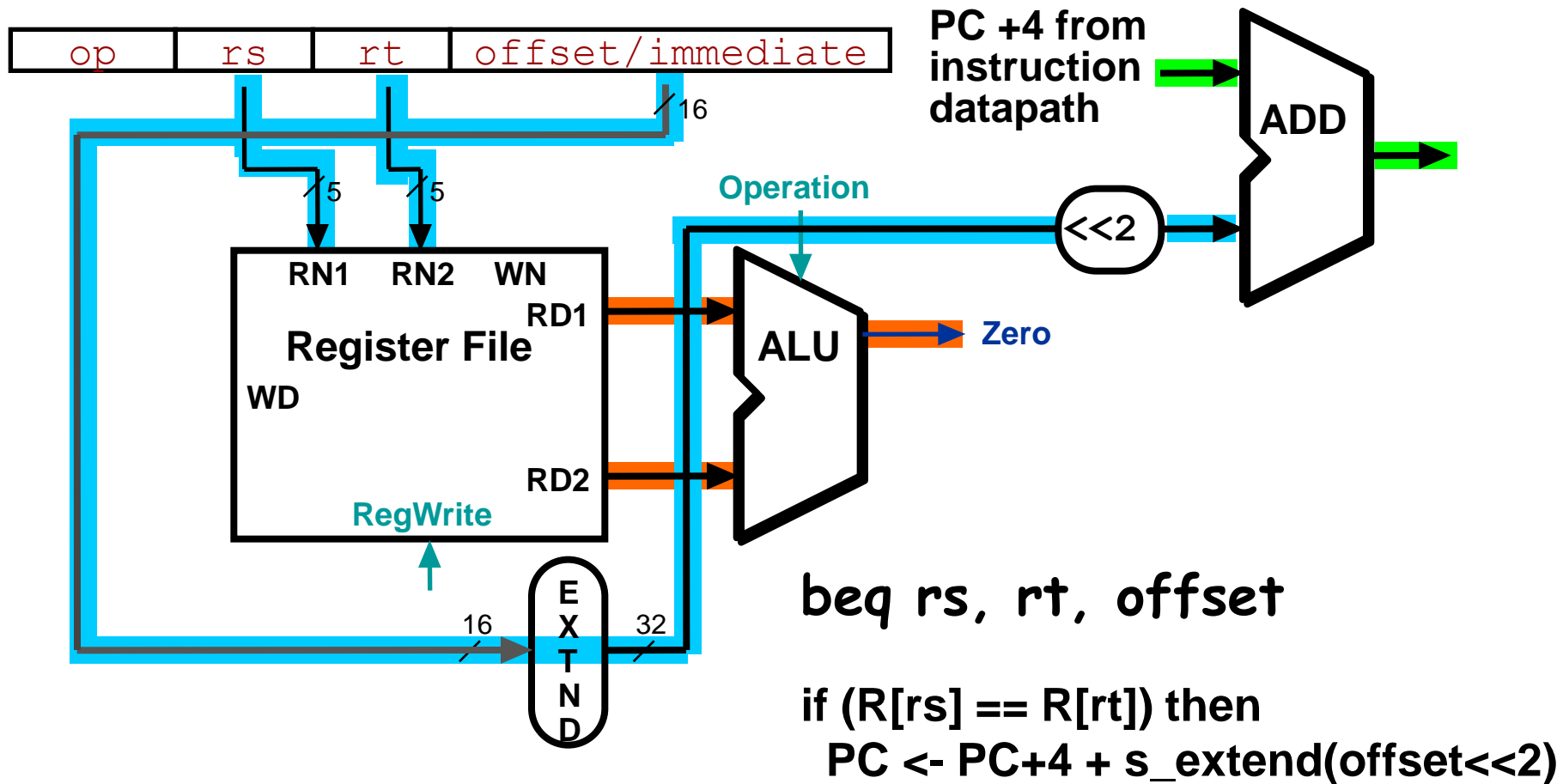


MIPS Datapath I: Single-Cycle

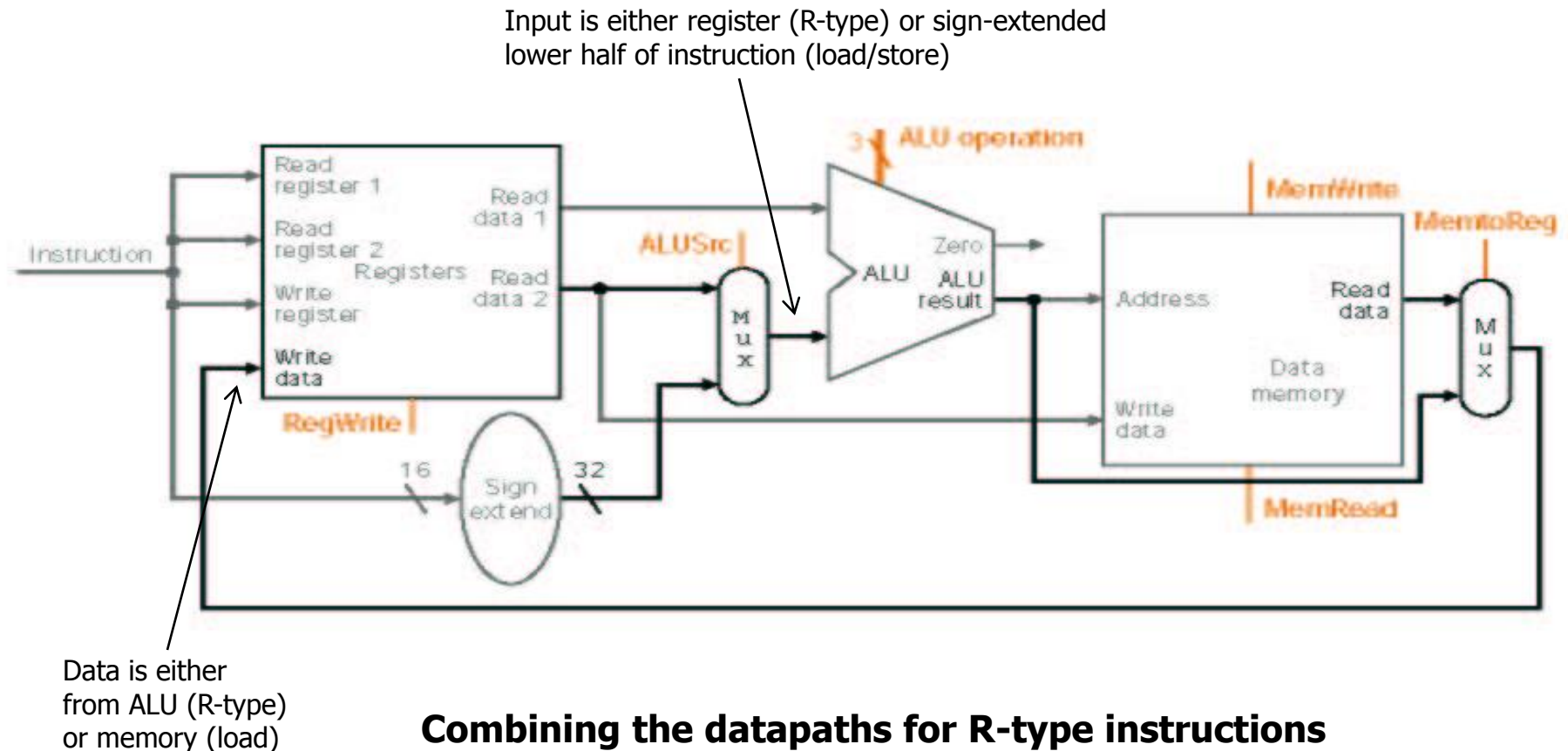


Combining the datapaths for R-type instructions and load/stores using two multiplexors

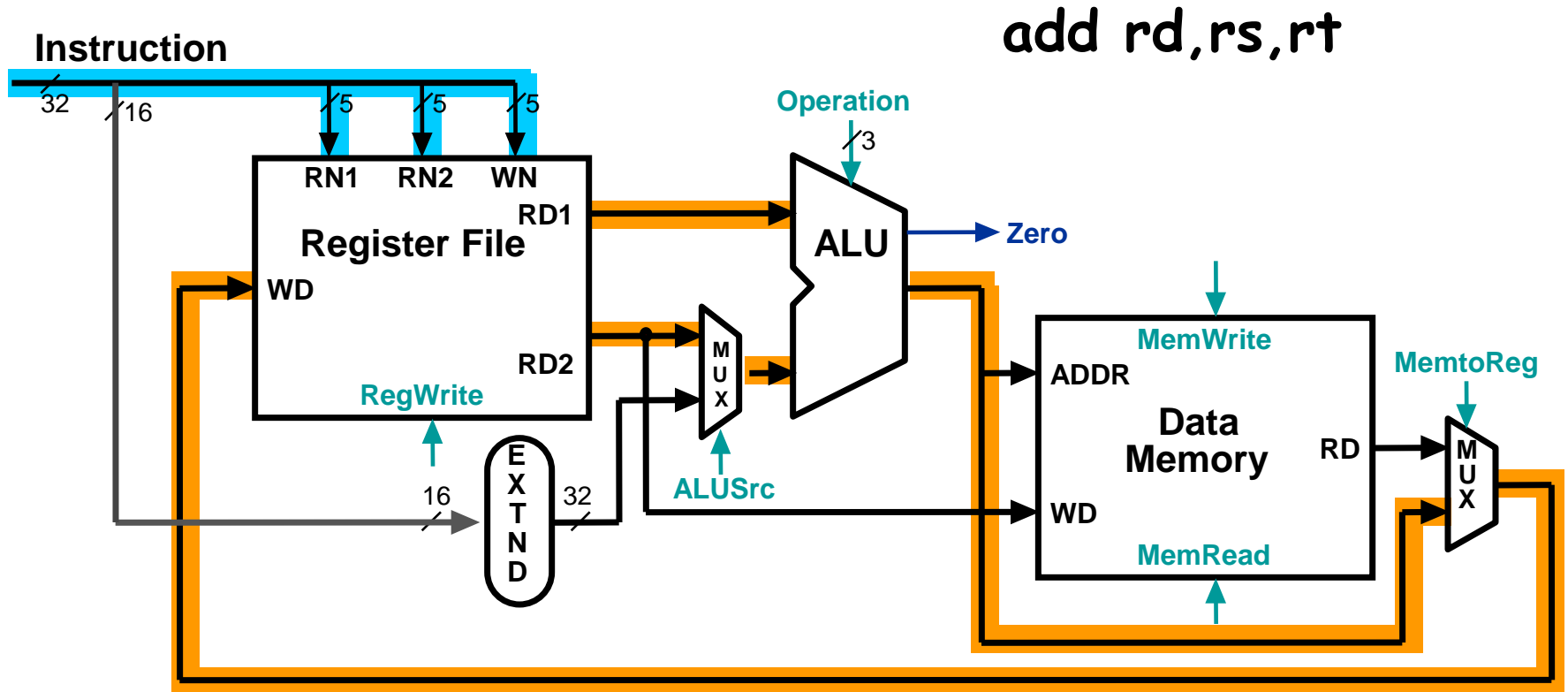Animating the Datapath: R-type Instruction




Animating the Datapath: Load Instruction


lw rt,offset(rs)

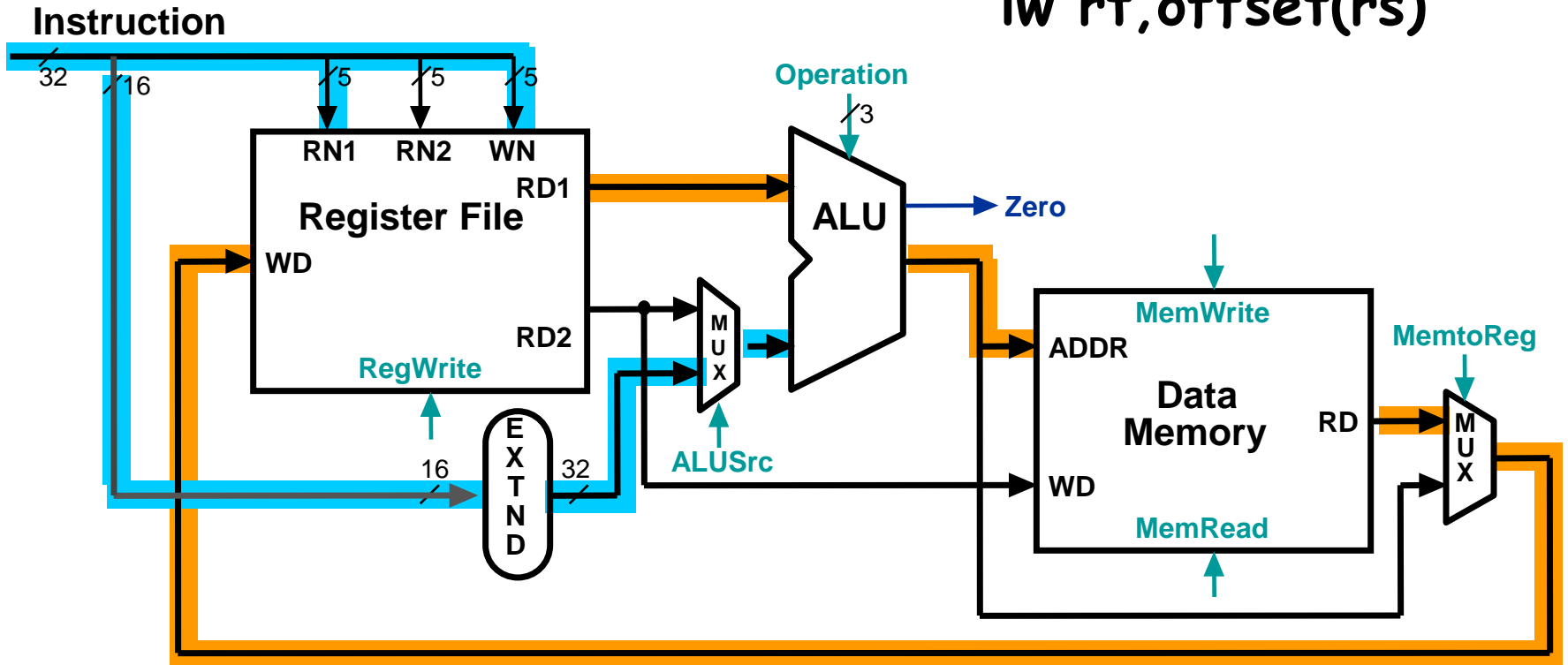

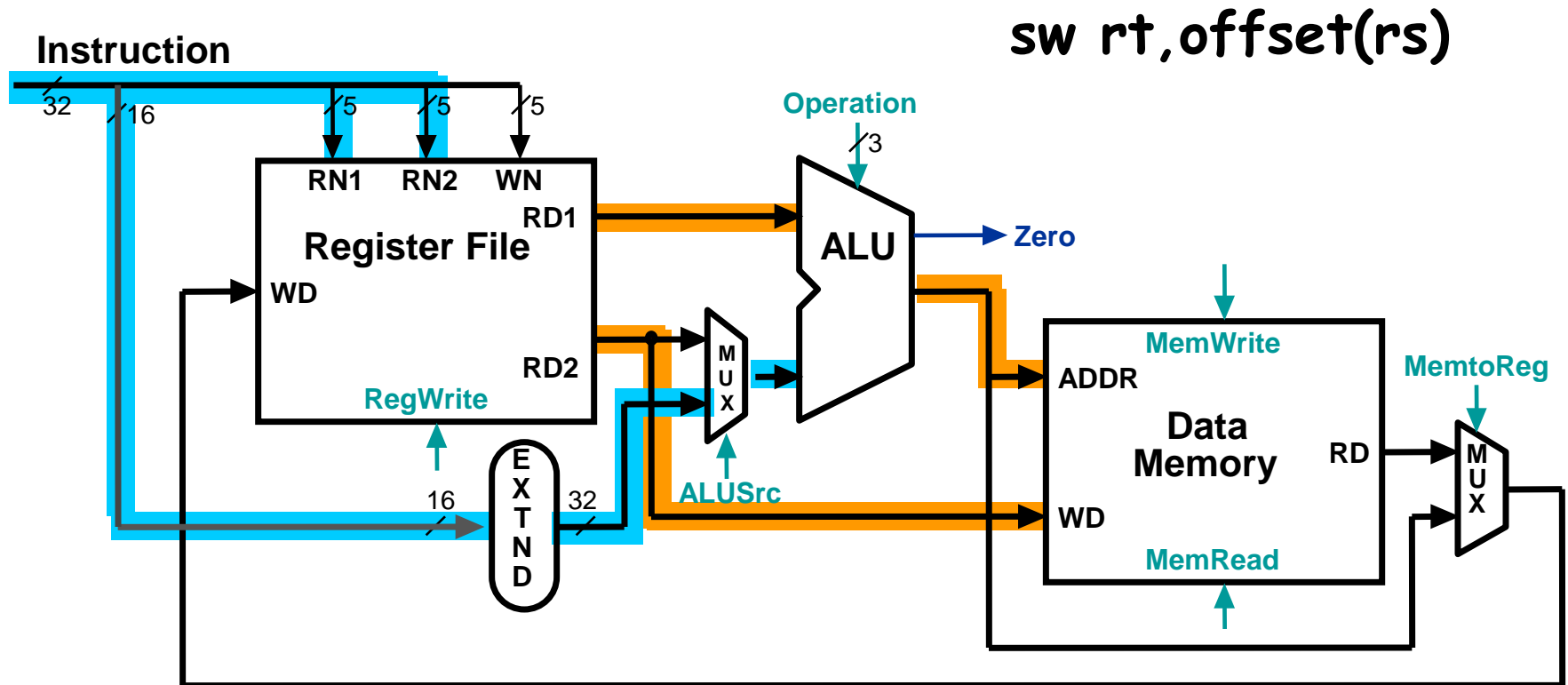
Animating the Datapath: Store Instruction



MIPS Datapath II: Single-Cycle

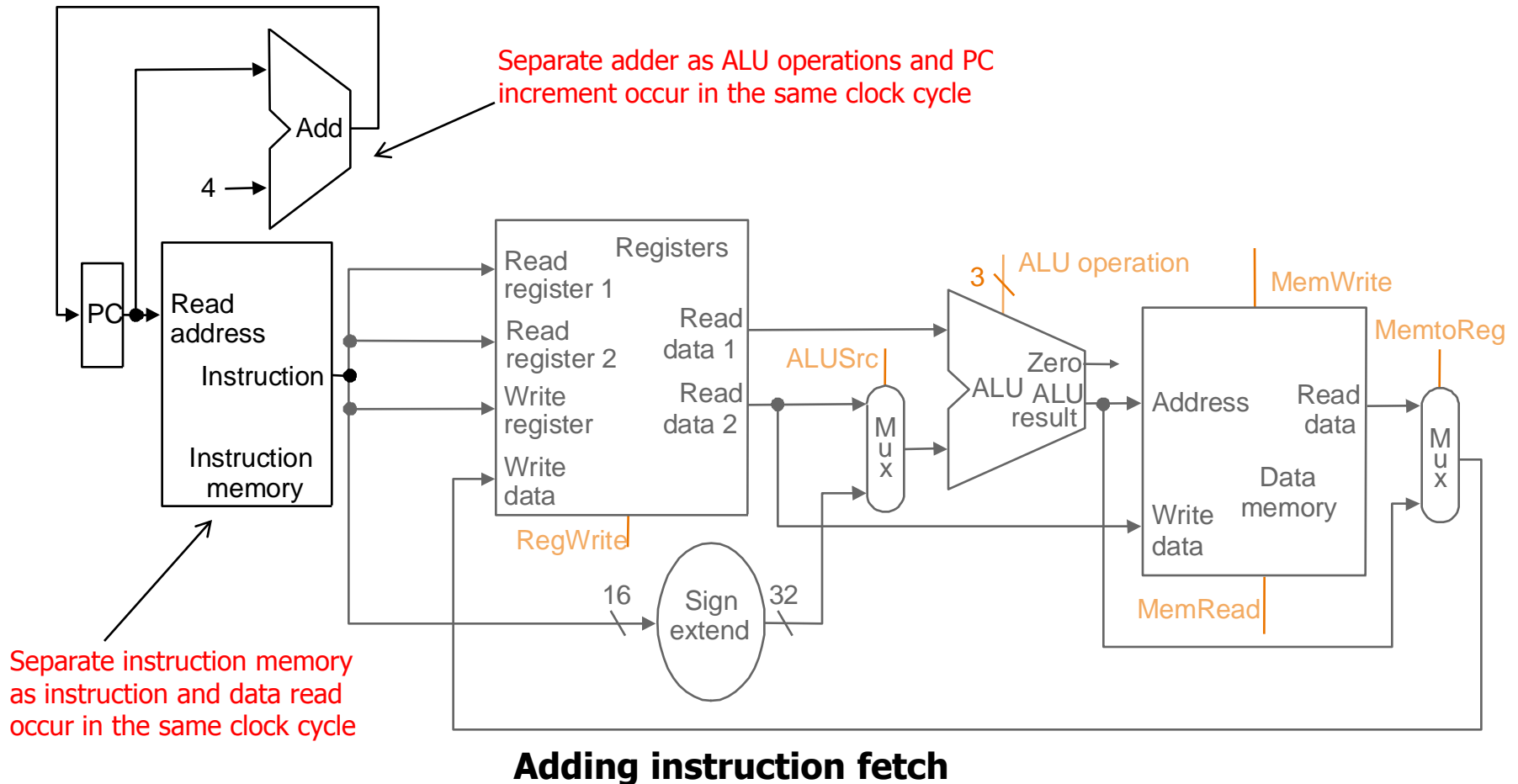


MIPS Datapath III: Single-Cycle

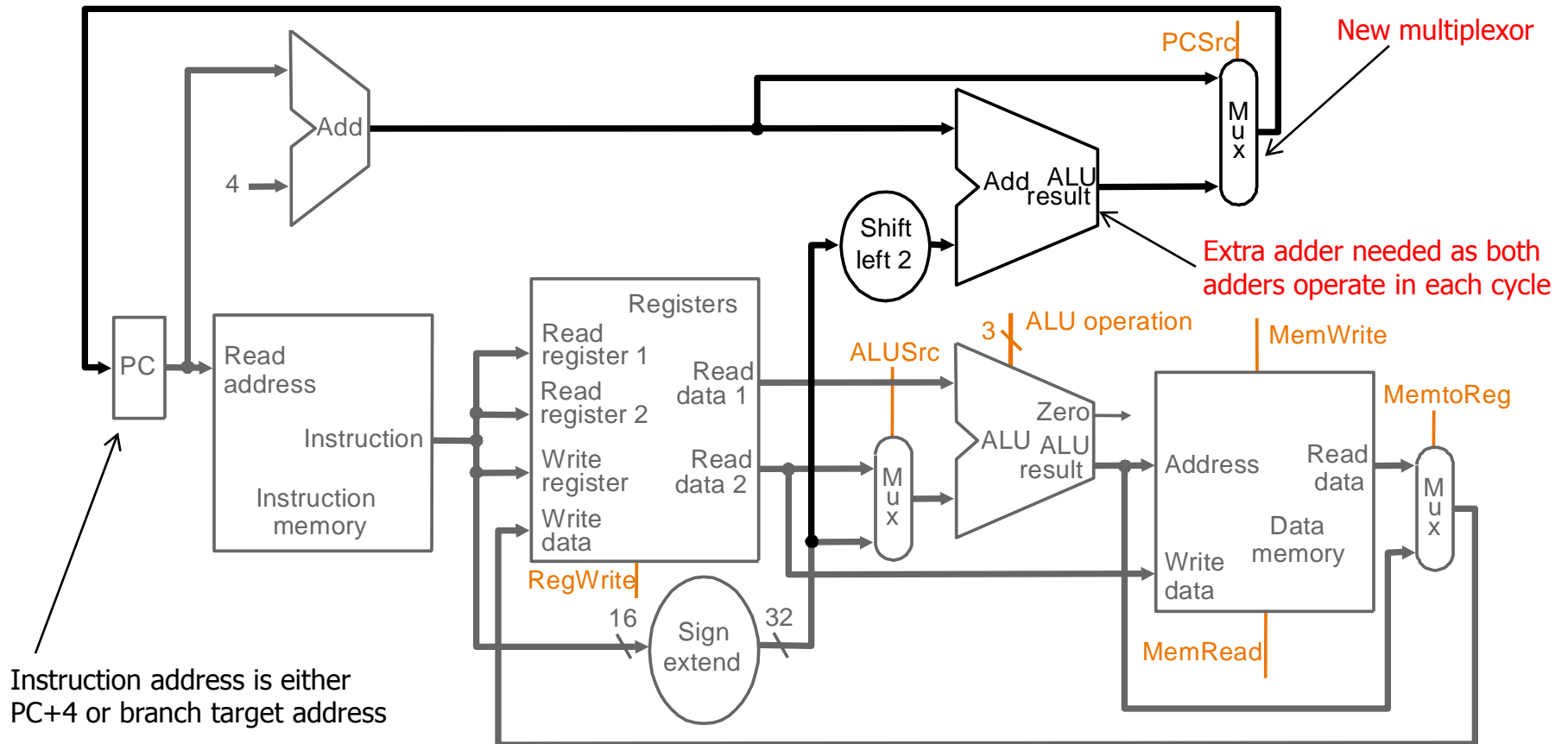

Adding branch capability and another multiplexor


Important note: in a single-cycle implementation data cannot be stored during an instruction – it only moves through combinational logic

Datapath Executing add

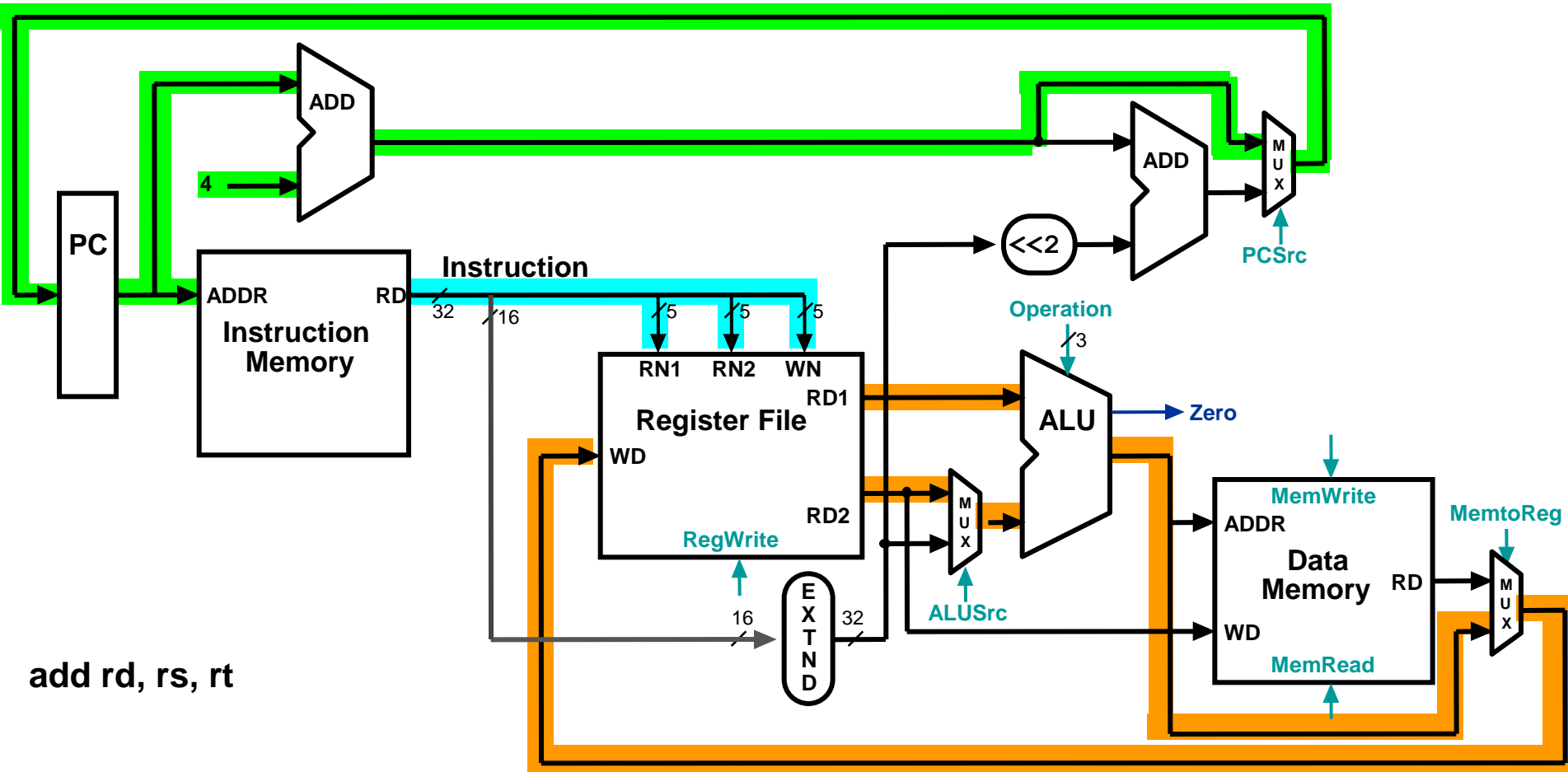


`add rd, rs, rt`

Datapath Executing lw

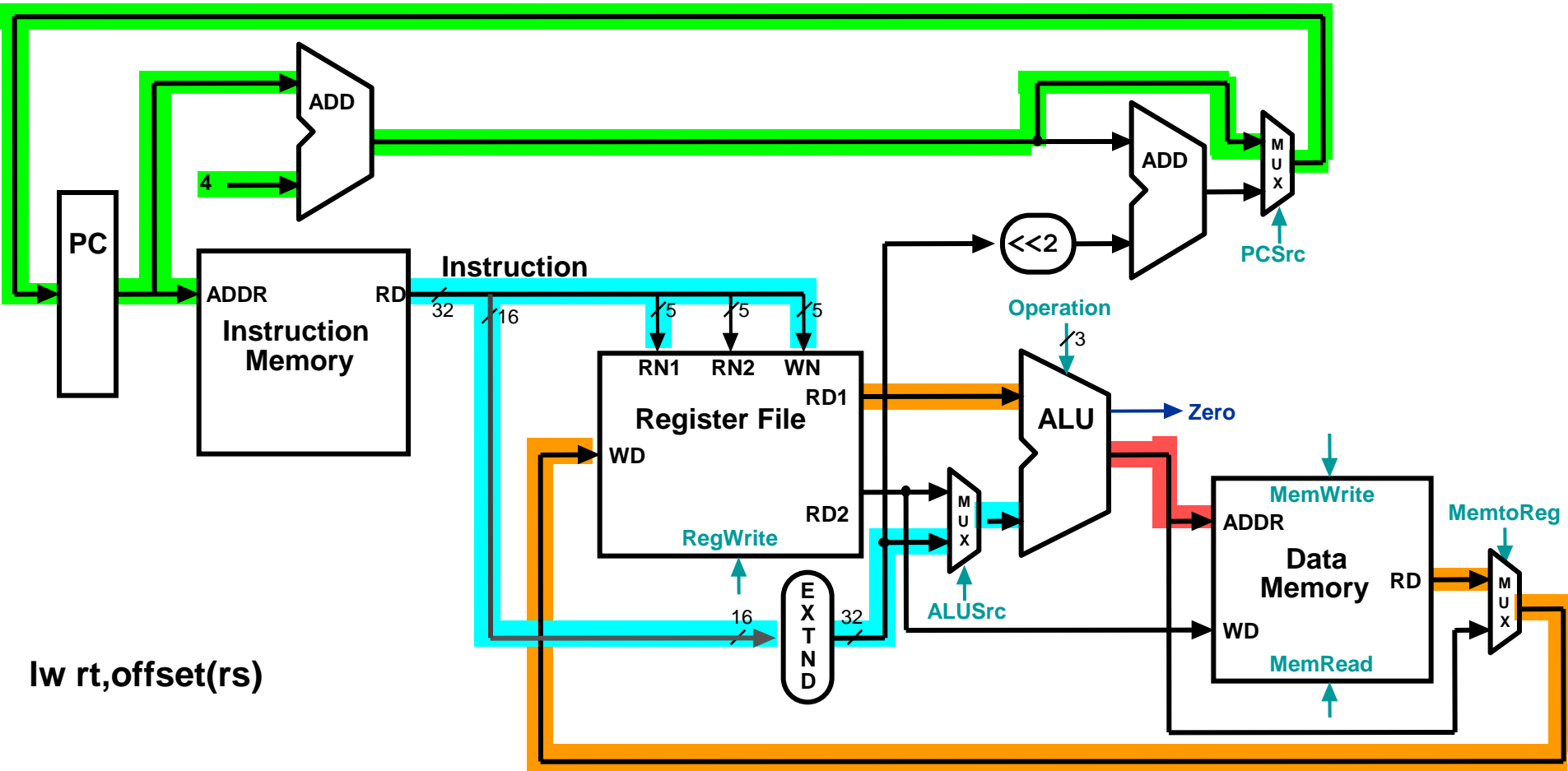

Datapath Executing sw

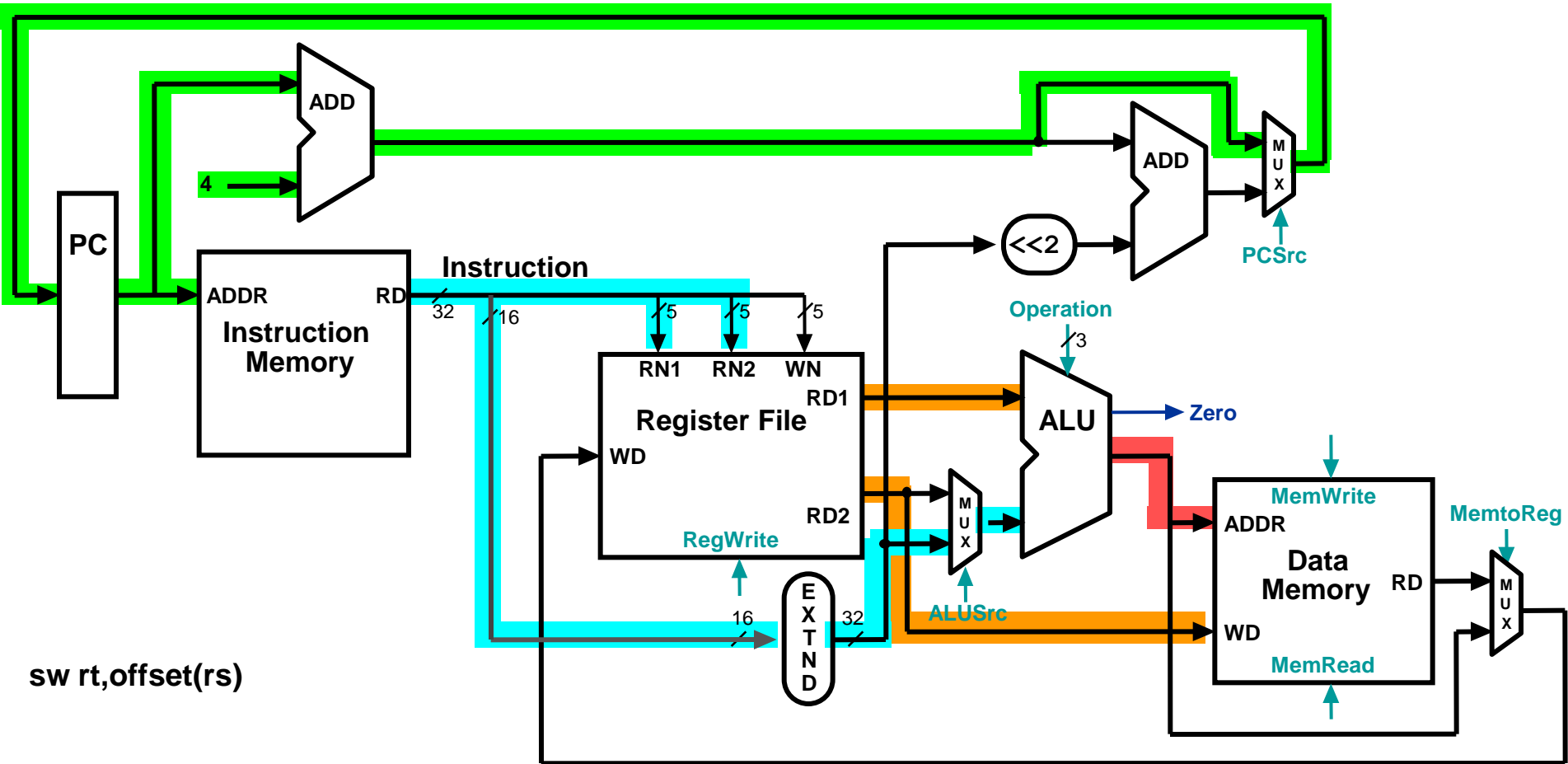

Datapath Executing `beq`

